

Sir Syed University of Engineering & Technology (SSUET)


Computer Engineering Department

Course Name: Basic Electronics

Semester: Spring 2011, 3rd

Batch: 2010(Sections: A,B)

Assignments # 2

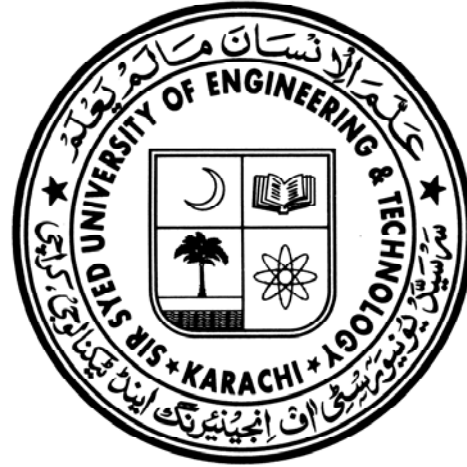

Course Responsible

Syed Hassan Raza Naqvi

Assistant Professor,

Computer Engineering Department

Office: STI,

SIR SYED UNIVERSITY OF ENGINEERING AND TECHNOLOGY
COMPUTER ENGINEERING DEPARTMENT
BASIC ELECTRONICS
2010 BATCH (Sections: A, B)
Last Submission Date: Announce in Class

Assignment #2

1. Series Diode Configuration with DC Inputs: Q5 – to – Q9
2. Parallel and Series Parallel Configuration: Q10 – to – Q13
3. Half Wave Rectification: Q22 – to – Q27
4. Full Wave Rectification: Q28 – to – Q31

Q5.

5. (a) $I = 0\text{mA}$; diode reverse-biased.

(b) $V_{20\Omega} = 20\text{V} - 0.7\text{V} = 19.3\text{V}$ (Kirchhoff's voltage law)

$$I = \frac{19.3\text{V}}{20\Omega} = 0.965\text{A}$$

(c) $I = \frac{10\text{V}}{10\Omega} = 1\text{A}$; center branch open

Q6.

(a) Diode forward-biased,

Kirchhoff's voltage law (cw): $-5\text{V} + 0.7\text{V} - V_o = 0$
 $V_o = -4.3\text{V}$

$$I_R = I_D = \frac{|V_o|}{R} = \frac{4.3\text{V}}{2.2\text{k}\Omega} = 1.955\text{mA}$$

(b) Diode forward-biased,

$$I_D = \frac{8\text{V} - 0.7\text{V}}{1.2\text{k}\Omega + 4.7\text{k}\Omega} = 1.24\text{mA}$$

$$V_o = V_{4.7\text{k}\Omega} + V_D = (1.24\text{mA})(4.7\text{k}\Omega) + 0.7\text{V} \\ = 6.53\text{V}$$

Q7.

$$7. (a) V_o = \frac{2k\Omega(20V - 0.7V - 0.3V)}{2k\Omega + 2k\Omega}$$

$$= \frac{1}{2}(20V - 1V) = \frac{1}{2}(19V) = \underline{9.5V}$$

$$(b) I = \frac{10V + 2V - 0.7V}{1.2k\Omega + 4.7k\Omega} = \frac{11.3V}{5.9k\Omega} = 1.915mA$$

$$V' = IR = (1.915mA)(4.7k\Omega) = 9V$$


$$V_o = V' - 2V = 9V - 2V = \underline{7V}$$

Q8.

8. (a) Determine the Thevenin equivalent circuit for the 10mA source and 2.2k Ω resistor.

$$E_{Th} = IR = (10mA)(2.2k\Omega) = 22V$$

$$R_{Th} = 2.2k\Omega$$

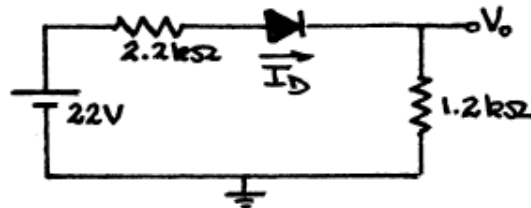

Diode forward-biased

$$I_D = \frac{22V - 0.7V}{2.2k\Omega + 1.2k\Omega} = \underline{6.26mA}$$

$$V_o = I_D(1.2k\Omega)$$

$$= (6.26mA)(1.2k\Omega)$$

$$= \underline{7.51V}$$

(b) Diode forward-biased

$$I_D = \frac{20V + 5V - 0.7V}{6.8k\Omega} = \underline{2.65mA}$$

Kirchhoff's voltage law: (CW)

$$+V_o - 0.7V + 5V = 0$$

$$V_o = \underline{-4.3V}$$

Q9.

$$(a) V_{o1} = 12V - 0.7V = \underline{11.3V}$$

$$V_{o2} = \underline{0.3V}$$

$$(b) V_{o1} = -10V + 0.3V + 0.7V = \underline{-9V}$$

$$I = \frac{10V - 0.7V - 0.3V}{1.2k\Omega + 3.3k\Omega} = \frac{9V}{4.5k\Omega} = 2mA, V_{o2} = -(2mA)(3.3k\Omega) = \underline{-6.6V}$$

Q10.

(a) Both diodes forward-biased.

$$I_R = \frac{20V - 0.7V}{4.7k\Omega} = 4.106mA$$

Assuming identical diodes:

$$I_D = \frac{I_R}{2} = \frac{4.106mA}{2} = \underline{2.05mA}$$

$$V_o = 20V - 0.7V = \underline{19.3V}$$

(b) Right diode forward-biased:

$$I_D = \frac{15V + 5V - 0.7V}{2.2k\Omega} = \underline{8.77mA}$$

$$V_o = 15V - 0.7V = \underline{14.3V}$$

Q11.

(a) Ge diode "on" preventing Si diode from turning "on".

$$I = \frac{10V - 0.3V}{1k\Omega} = \frac{9.7V}{1k\Omega} = \underline{9.7mA}$$

$$V_o = 10V - 0.3V = \underline{9.7V}$$

$$(b) I = \frac{16V - 0.7V - 0.7V - 12V}{4.7k\Omega} = \frac{2.6V}{4.7k\Omega} = \underline{0.553mA}$$

$$V_o = 12V + (0.553mA)(4.7k\Omega) = \underline{14.6V}$$

Q12.

Both diodes forward-biased,

$$V_{o1} = \underline{0.7V}, V_{o2} = \underline{0.3V}$$


$$I_{1k\Omega} = \frac{20V - 0.7V}{1k\Omega} = \frac{19.3V}{1k\Omega} = 19.3mA$$

$$I_{0.47k\Omega} = \frac{0.7V - 0.3V}{0.47k\Omega} = 0.851mA$$

$$\begin{aligned} I(\text{Si diode}) &= I_{1k\Omega} - I_{0.47k\Omega} \\ &= 19.3mA - 0.851mA \\ &= \underline{18.45mA} \end{aligned}$$

Q13.

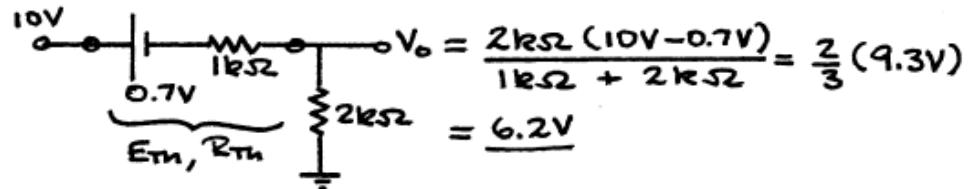3. For the parallel Si- $2k\Omega$ branches a Thevenin equivalent will result (for "on" diodes) in a single series branch of $0.7V$ and $1k\Omega$ resistor as shown below:





$$I_{2k\Omega} = \frac{6.2V}{2k\Omega} = 3.1mA$$

$$I_D = \frac{I_{2k\Omega}}{2} = \frac{3.1mA}{2} = 1.55mA$$

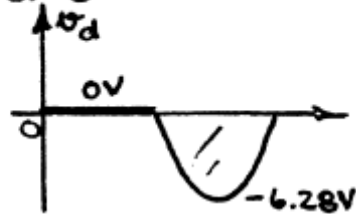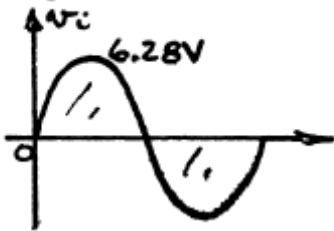Q22.

$$V_{dc} = 0.318 V_m \Rightarrow V_m = \frac{V_{dc}}{0.318} = \frac{2V}{0.318} = 6.28V$$







Q23.

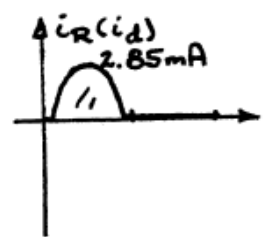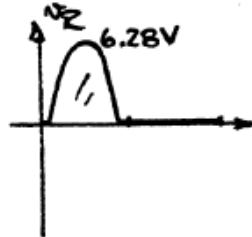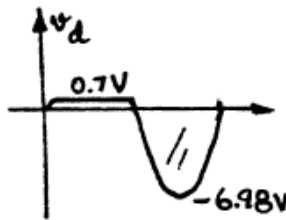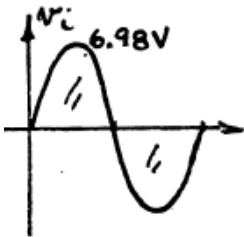23. Using $V_{dc} \cong 0.318 (V_m - V_T)$



$$2V = 0.318 (V_m - 0.7V)$$

Solving: $V_m = 6.98V \cong 10:1$ for $V_m:V_T$




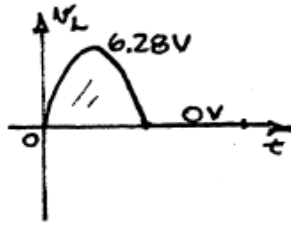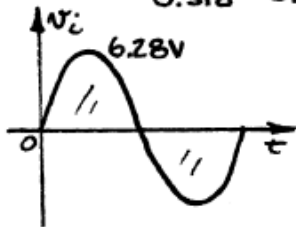Q24.

$$24. \quad V_m = \frac{V_{dc}}{0.318} = \frac{2V}{0.318} = 6.28V$$



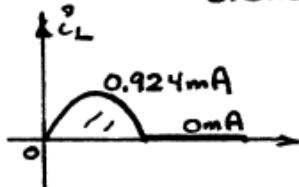
$$I_{Lmax} = \frac{6.28V}{6.8k\Omega} = 0.924mA$$



$$I_{max}(2.2k\Omega) = \frac{6.28V}{2.2k\Omega} = 2.855mA$$

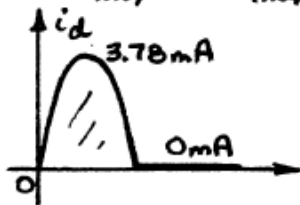
$$I_{Dmax} = I_{Lmax} + I_{max}(2.2k\Omega) = 0.924mA + 2.855mA = 3.78mA$$



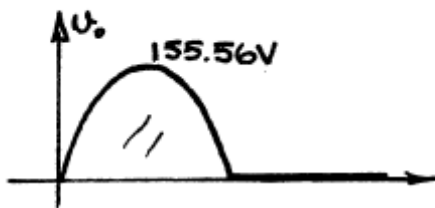Q25.

$$V_m = \sqrt{2} 110V = 155.56V$$

$$V_{dc} = 0.318 V_m = 0.318(155.56V) = \underline{49.47V}$$



Q26.

• Diode will conduct when $V_o = 0.7V$, That is,

$$V_o = 0.7V = \frac{10k\Omega(V_i)}{10k\Omega + 1k\Omega}$$

$$\text{Solving: } V_i = 0.77V$$


For $V_i \geq 0.77V$ Si diode is "on" and $V_o = 0.7V$

For $V_i < 0.77V$ Si diode open and level of V_o determined by voltage divider rule:

$$V_o = \frac{10k\Omega(V_i)}{10k\Omega + 1k\Omega} = 0.909V_i$$

For $V_i = -10V$:


$$V_o = 0.909(-10V) = -9.09V$$

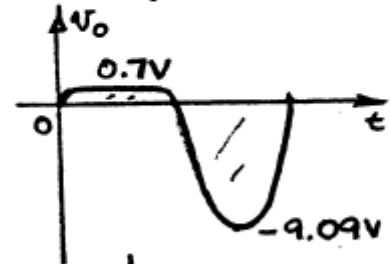

When $V_o = 0.7V$, $V_{R_{max}} = V_{i_{max}} - 0.7V = 10V - 0.7V = 9.3V$

$$I_{R_{max}} = \frac{9.3V}{1k\Omega} = 9.3mA$$
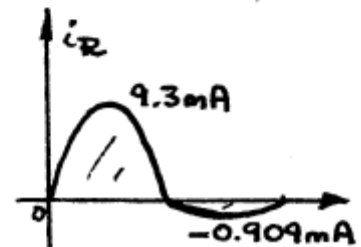
$$I_{max}(\text{reverse}) = \frac{10V}{1k\Omega + 10k\Omega} = 0.909mA$$



Q27.

(a) $P_{max} = 14mW = (0.7V)I_D$

$$I_D = \frac{14mW}{0.7V} = 20mA$$

(b) $4.7k\Omega \parallel 56k\Omega = 4.34k\Omega$

$$V_R = 160V - 0.7V = 159.3V$$

$$I_{max} = \frac{159.3V}{4.34k\Omega} = 36.71mA$$

(c) $I_{diode} = \frac{I_{max}}{2} = \frac{36.71mA}{2} = 18.36mA$

(d) yes $I_D = 20mA > 18.36mA$

(e) $I_{diode} = 36.71mA \gg I_{max} = 20mA$

Q28.

$$(a) V_m = \sqrt{2}(120V) = 169.7V$$

$$V_{Lm} = V_{im} - 2V_D$$

$$= 169.7V - 2(0.7V) = 169.7V - 1.4V$$

$$= 168.3V$$


$$V_{dc} = 0.636(168.3V) = \underline{107.04V}$$

$$(b) PIV = V_m(\text{load}) + V_D = 168.3V + 0.7V = \underline{169V}$$

$$(c) I_D(\text{max}) = \frac{V_{Lm}}{R_L} = \frac{168.3V}{1k\Omega} = \underline{168.3mA}$$

$$(d) P_{max} = V_D I_D = (0.7V) I_{max}$$
$$= (0.7V)(168.3mA)$$
$$= \underline{117.81mW}$$


Q29.

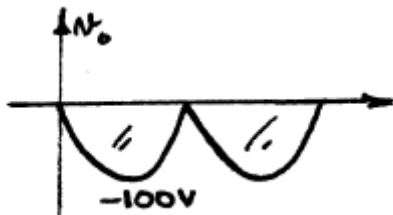

$$PIV = \underline{100V}$$

Q30.

Positive half-cycle of V_i :

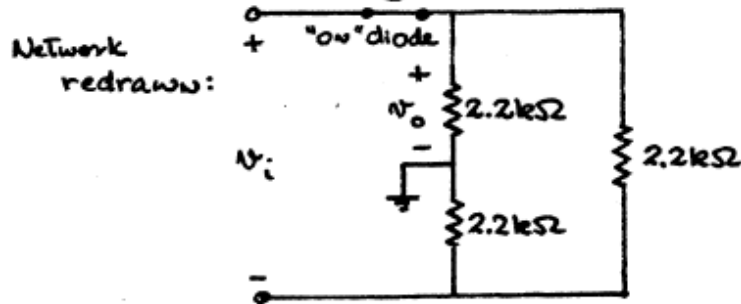

Voltage-divider rule:


$$V_{o\max} = \frac{2.2\text{k}\Omega (V_{i\max})}{2.2\text{k}\Omega + 2.2\text{k}\Omega}$$

$$= \frac{1}{2} (V_{i\max})$$

$$= \frac{1}{2} (100\text{V})$$

$$= \underline{50\text{V}}$$

Negative half-cycle of V_i :

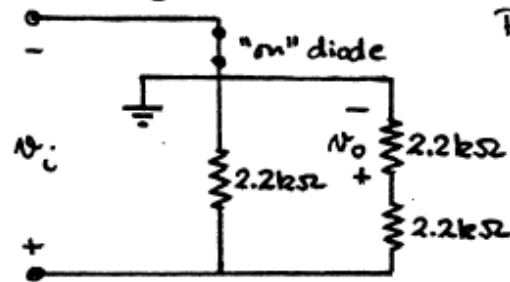

Polarity of V_o across the $2.2\text{k}\Omega$ resistor acting as a load is the same.


Voltage-divider rule:

$$V_{o\max} = \frac{2.2\text{k}\Omega (V_{i\max})}{2.2\text{k}\Omega + 2.2\text{k}\Omega}$$

$$= \frac{1}{2} (V_{i\max})$$

$$= \frac{1}{2} (100\text{V})$$

$$= \underline{50\text{V}}$$

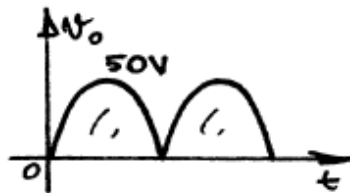

$$V_{dc} = 0.636 V_m = 0.636 (50\text{V})$$

$$= \underline{31.8\text{V}}$$

Q31.

Positive pulse of V_i :

Top left diode "off", bottom left diode "on"

$$2.2\text{k}\Omega \parallel 2.2\text{k}\Omega = 1.1\text{k}\Omega$$

$$V_{o\text{peak}} = \frac{1.1\text{k}\Omega (170\text{V})}{1.1\text{k}\Omega + 2.2\text{k}\Omega} = 56.67\text{V}$$

Negative pulse of V_i :

Top left diode "on", bottom left diode "off"

$$V_{o\text{peak}} = \frac{1.1\text{k}\Omega (170\text{V})}{1.1\text{k}\Omega + 2.2\text{k}\Omega} = 56.67\text{V}$$

$$V_{dc} = 0.636 (56.67\text{V}) = \underline{36.04\text{V}}$$