

Sir Syed University of Engineering & Technology (SSUET)


Computer Engineering Department

Course Name: Basic Electronics

Semester: Spring 2011, 3rd

Batch: 2010(Sections: A,B)

Assignments # 4

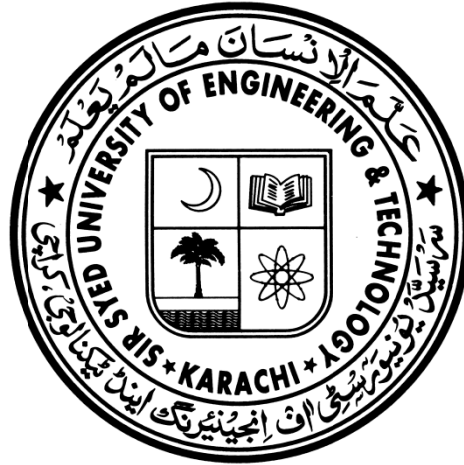

Course Responsible

Syed Hassan Raza Naqvi

Assistant Professor,

Computer Engineering Department

Office: STI,

SIR SYED UNIVERSITY OF ENGINEERING AND TECHNOLOGY
 COMPUTER ENGINEERING DEPARTMENT
 BASIC ELECTRONICS
 2010 BATCH (Sections: A, B)
 Last Submission Date: 17th MARCH, 2011, 4PM.

Assignment Solution #4

1. Clamper: Q37 – to – Q41

Q37.


37(a) Starting with $V_i = -20V$, the diode is in the "on" state and the capacitor quickly charges to $-20V$. During this interval of time V_o is across the "on" diode (short-circuit equivalent) and $V_o = 0V$.

When V_i switches to the $+20V$ level the diode enters the "off" state (open-circuit equivalent) and $V_o = V_i + V_C = 20V + 20V = +40V$.



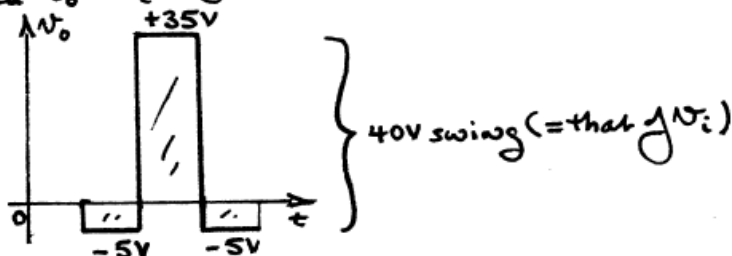(b) Starting with $V_i = -20V$, the diode is in the "on" state and the capacitor quickly charges up to $-15V$. Note that $V_i = +20V$ and the $5V$ supply are additive across the capacitor. During this time interval V_o is across "on" diode and $5V$ supply and $V_o = -5V$.


When V_i switches to the $+20V$ level the diode enters the "off" state and $V_o = V_i + V_C = 20V + 15V = 35V$.



Q38.

38. (a) For negative half cycle capacitor charges to peak value of $120V - 0.7V = 119.3V$ with polarity $(- \text{---} | \text{---} +)$. The output V_o is directly across the "on" diode resulting in $V_o = -0.7V$ as a negative peak value.

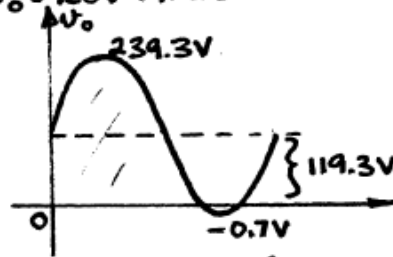
For the next positive half cycle $V_o = V_i + 119.3V$ with a peak value of $V_o = 120V + 119.3V = 239.3V$.



↑ vertical shift of $119.3V$

(b) For positive half cycle capacitor charges to peak value of $120V - 20V - 0.7V = 99.3V$ with polarity $(+ \text{---} | \text{---} -)$. The output $V_o = 20V + 0.7V = 20.7V$

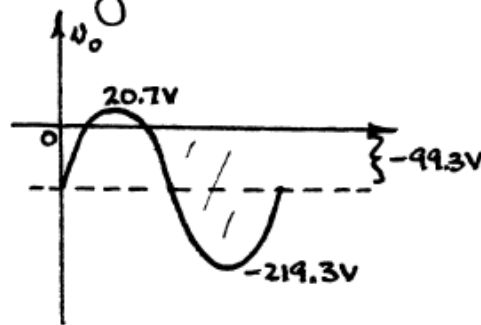For next negative half cycle $V_o = V_i - 99.3V$ with negative peak value of $V_o = -120V - 99.3V = -219.3V$



↓ vertical shift of $-99.3V$

Using the ideal diode approximation the vertical shift of part (a) would be $120V$ rather than $119.3V$ and $-100V$ rather than $-99.3V$ for part (b). Using the ideal diode approximation would certainly be appropriate in this case.

Q39.

39. (a) $\tau = RC = (56k\Omega)(0.1\mu F) = 5.6ms$
 $5\tau = 28ms$

(b) $5\tau = 28ms \gg \frac{T}{2} = \frac{1ms}{2} = 0.5ms$, 56:1


(c) Positive pulse of v_i :

Diode "on" and $v_o = -2V + 0.7V = -1.3V$

Capacitor charges to $10V + 2V - 0.7V = 11.3V$

Negative pulse of v_i :

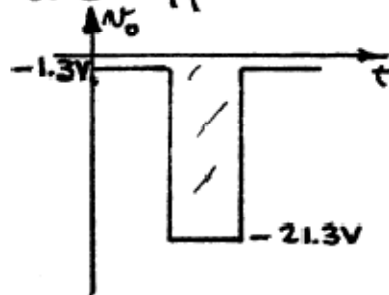Diode "off" and $v_o = -10V - 11.3V = -21.3V$




Q40.

40. Solution is network of Fig. 2.159(b) using a 10V supply in place of the 5V source.

Q41.

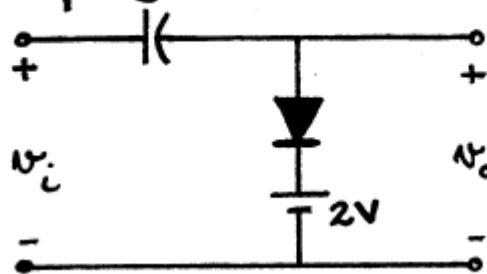41. Network of Fig. 2.161 with 2V battery reversed.



2. Zener Diode: Q42 – to – Q46

Q42.

42. (a) In the absence of the Zener diode

$$V_L = \frac{180\Omega(20V)}{180\Omega + 220\Omega} = 9V$$

$V_L = 9V < V_Z = 10V$ and diode non-conducting

$$\text{Therefore, } I_L = I_R = \frac{20V}{220\Omega + 180\Omega} = \underline{50mA}$$

$$\text{with } I_Z = \underline{0mA}$$

$$\text{and } V_L = \underline{9V}$$

(b) In the absence of the Zener diode

$$V_L = \frac{470\Omega(20V)}{470\Omega + 220\Omega} = 13.62V$$

$V_L = 13.62 > V_Z = 10V$ and Zener diode "on"

Therefore $V_L = \underline{10V}$ and $V_{R_s} = 10V$

$$I_{R_s} = V_{R_s}/R_s = 10V/220\Omega = \underline{45.45mA}$$

$$I_L = V_L/R_L = 10V/470\Omega = \underline{21.28mA}$$

$$\text{and } I_Z = I_{R_s} - I_L = 45.45mA - 21.28mA = \underline{24.17mA}$$

$$(c) P_{Z_{max}} = 400mW = V_Z I_Z = (10V) I_Z$$

$$I_Z = \frac{400mW}{10V} = 40mA$$

$$I_{L_{min}} = I_{R_s} - I_{Z_{max}} = 45.45mA - 40mA = 5.45mA$$

$$R_L = \frac{V_L}{I_{L_{min}}} = \frac{10V}{5.45mA} = \underline{1,834.86\Omega}$$

Large R_L reduces I_L and forces more of I_{R_s} to pass through Zener diode.

(d) In the absence of the Zener diode

$$V_L = 10V = \frac{R_L(20V)}{R_L + 220\Omega}$$

$$10R_L + 2200 = 20R_L$$

$$10R_L = 2200$$

$$R_L = \underline{220\Omega}$$

Q43.

$$43. (a) V_Z = 12V, R_L = \frac{V_L}{I_L} = \frac{12V}{200mA} = 60\Omega$$

$$V_L = V_Z = 12V = \frac{R_L V_i}{R_L + R_s} = \frac{60\Omega (16V)}{60\Omega + R_s}$$

$$720 + 12R_s = 960$$

$$12R_s = 240$$

$$R_s = 20\Omega$$

$$(b) P_{Zmax} = V_Z I_{Zmax}$$

$$= (12V)(200mA)$$

$$= 2.4W$$

Q44.

44. Since $I_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L}$ is fixed in magnitude the maximum value of I_{R_s} will occur when I_Z is a maximum. The maximum level of I_{R_s} will in turn determine the maximum permissible level of V_i .

$$I_{Zmax} = \frac{P_{Zmax}}{V_Z} = \frac{400mW}{8V} = 50mA$$

$$I_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L} = \frac{8V}{220\Omega} = 36.36mA$$

$$I_{R_s} = I_Z + I_L = 50mA + 36.36mA = 86.36mA$$

$$I_{R_s} = \frac{V_i - V_Z}{R_s}$$

$$\text{or } V_i = I_{R_s} R_s + V_Z$$

$$= (86.36mA)(91\Omega) + 8V = 7.86V + 8V = 15.86V$$

Any value of V_i that exceeds 15.86V will result in a current I_Z that will exceed the maximum value.

Q45.

45. At 30V we have to be sure Zener diode is "on"

$$\therefore V_L = 20V = \frac{R_L V_i}{R_L + R_s} = \frac{1k\Omega (30V)}{1k\Omega + R_s}$$

$$\text{Solving, } R_s = 0.5k\Omega$$

$$\text{At } 50V \quad I_{R_s} = \frac{50V - 20V}{0.5k\Omega} = 60mA, \quad I_L = \frac{20V}{1k\Omega} = 20mA$$

$$I_{ZM} = I_{R_s} - I_L = 60mA - 20mA = 40mA$$

Q46.

46. For $v_i = +50V$:

Z_1 forward-biased at $0.7V$

Z_2 reverse-biased at the Zener potential and $V_{Z_2} = 10V$.


Therefore, $V_o = V_{Z_1} + V_{Z_2} = 0.7V + 10V = \underline{10.7V}$

For $v_i = -50V$:


Z_1 reverse-biased at the Zener potential and $V_{Z_1} = -10V$.

Z_2 forward-biased at $-0.7V$

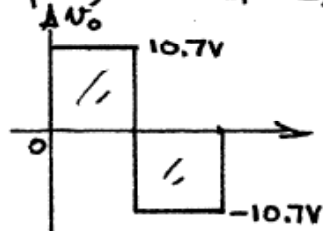Therefore, $V_o = V_{Z_1} + V_{Z_2} = \underline{-10.7V}$



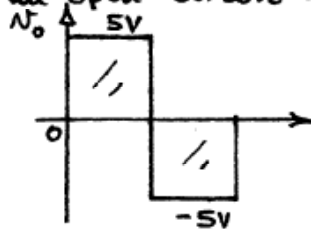For a $5V$ -square wave neither Zener diode will reach its Zener potential. In fact, for either polarity of v_i one Zener diode will be in an open-circuit state resulting in $v_o = v_i$.



3. Voltage Multiplier: Q47 – to – Q48

Q47.

$$47. V_m = 1.414(120V) = 169.68V$$

$$2V_m = 2(169.68V) = \underline{339.36V}$$

Q48.

48. The PIV for each diode is $2V_m$

$$\therefore PIV = 2(1.414)(V_{rms})$$