

# Sir Syed University of Engineering & Technology (SSUET)


Computer Engineering Department

*Course Name: Basic Electronics*

*Semester: Spring 2011, 3<sup>rd</sup>*

*Batch: 2010(Sections: A,B)*

## Assignments # 6

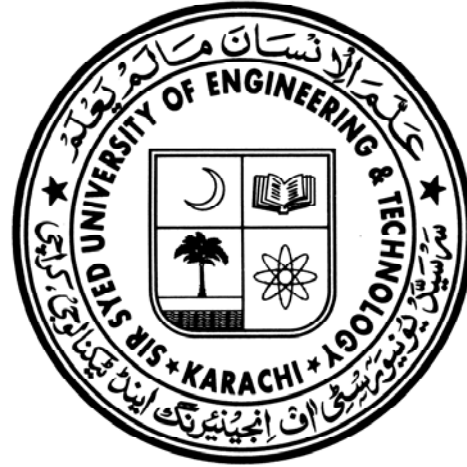

Course Responsible

*Syed Hassan Raza Naqvi*

Assistant Professor,  
Computer Engineering Department  
Office: STI,

SIR SYED UNIVERSITY OF ENGINEERING AND TECHNOLOGY  
COMPUTER ENGINEERING DEPARTMENT

BASIC ELECTRONICS

2010 BATCH (Sections: A, B)

Last Submission Date: 11<sup>th</sup> May, 2011.

**Assignment # 6**

Q1. For the fixed-bias configuration of Fig. 4.1, determine:

- (a)  $I_{BQ}$ .
- (b)  $I_{CQ}$ .
- (c)  $V_{CEQ}$ .
- (d)  $V_C$ .
- (e)  $V_B$ .
- (f)  $V_E$ .

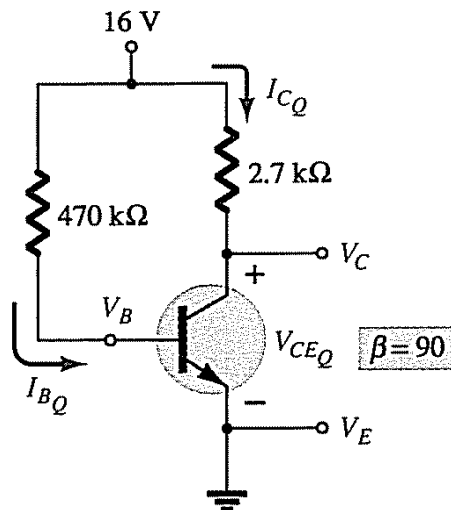


Figure 4.1 Problems 1, and 4.

(a)  $I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B} = \frac{16V - 0.7V}{470k\Omega} = \frac{15.3V}{470k\Omega} = \underline{32.55\mu A}$

(b)  $I_{CQ} = \beta I_{BQ} = (90)(32.55\mu A) = \underline{2.93mA}$

(c)  $V_{CEQ} = V_{CC} - I_{CQ} R_C = 16V - (2.93mA)(2.7k\Omega) = \underline{8.09V}$

(d)  $V_C = V_{CEQ} = \underline{8.09V}$

(e)  $V_B = V_{BE} = \underline{0.7V}$

(f)  $V_E = \underline{0V}$

---

Q2. Given the information appearing in Fig. 4.2, determine:

- (a)  $I_C$ .
- (b)  $R_C$ .
- (c)  $R_B$ .
- (d)  $V_{CE}$ .

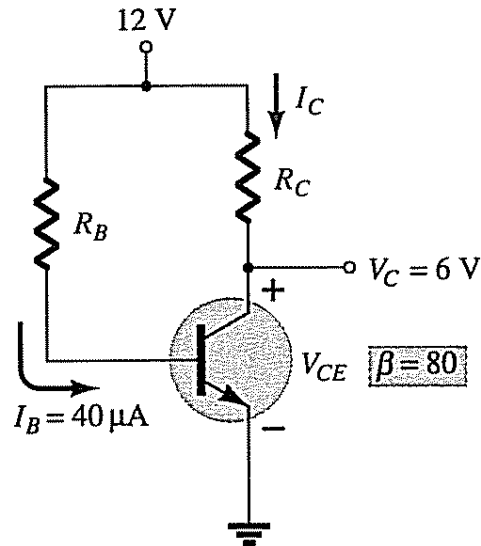


Figure 4.2 Problems 2.

$$(a) I_C = \beta I_B = 80(40 \mu\text{A}) = \underline{3.2\text{mA}}$$

$$(b) R_C = \frac{V_{R_C}}{I_C} = \frac{V_{CC} - V_C}{I_C} = \frac{12\text{V} - 6\text{V}}{3.2\text{mA}} = \frac{6\text{V}}{3.2\text{mA}} = \underline{1.875\text{k}\Omega}$$

$$(c) R_B = \frac{V_{R_B}}{I_B} = \frac{12\text{V} - 0.7\text{V}}{40 \mu\text{A}} = \frac{11.3\text{V}}{40 \mu\text{A}} = \underline{282.5\text{k}\Omega}$$

$$(d) V_{CE} = V_C = \underline{6\text{V}}$$

Q3. Given the information appearing in Fig. 4.3, determine:

- (a)  $I_C$ .
- (b)  $V_{CC}$ .
- (c)  $\beta$ .
- (d)  $R_B$ .

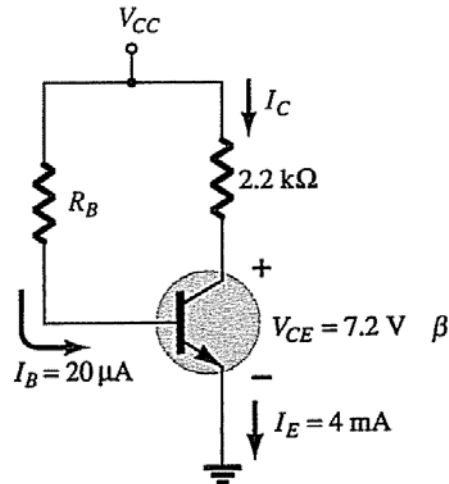


Figure 4.3 Problems 3.

$$(a) I_C = I_E - I_B = 4\text{mA} - 20\mu\text{A} = \underline{3.98\text{mA}} \approx 4\text{mA}$$

$$(b) V_{CC} = V_{CE} + I_C R_C = 7.2\text{V} + (3.98\text{mA})(2.2\text{k}\Omega) \\ = \underline{15.96\text{V}} \approx 16\text{V}$$

$$(c) \beta = \frac{I_C}{I_B} = \frac{3.98\text{mA}}{20\mu\text{A}} = \underline{199} \approx 200$$

$$(d) R_B = \frac{V_{R_B}}{I_B} = \frac{V_{CC} - V_{BE}}{I_B} = \frac{15.96\text{V} - 0.7\text{V}}{20\mu\text{A}} = \underline{763\text{k}\Omega}$$

Q4. Find the saturation current ( $I_{C_{sat}}$ ) for the fixed-bias configuration of Fig. 4.1.

$$I_{C_{sat}} = \frac{V_{CC}}{R_C} = \frac{16\text{V}}{2.7\text{k}\Omega} = \underline{5.93\text{mA}}$$

Q5. Given the BJT transistor characteristics of Fig. 4.4:

- Draw a load line on the characteristics determined by  $E = 21\text{ V}$  and  $R_C = 3\text{ k}\Omega$  for a fixed-bias configuration.
- Choose an operating point midway between cutoff and saturation. Determine the value of  $R_B$  to establish the resulting operating point.
- What are the resulting values of  $I_{CQ}$  and  $V_{CEQ}$ ?
- What is the value of  $\beta$  at the operating point?
- What is the value of  $\alpha$  defined by the operating point?
- What is the saturation ( $I_{Csat}$ ) current for the design?
- Sketch the resulting fixed-bias configuration.
- What is the dc power dissipated by the device at the operating point?
- What is the power supplied by  $V_{CC}$ ?
- Determine the power dissipated by the resistive elements by taking the difference between the results of parts (h) and (i).

(a) Load line intersects vertical axis at  $I_C = \frac{21\text{V}}{3\text{k}\Omega} = 7\text{mA}$  and horizontal axis at  $V_{CE} = 21\text{V}$

$$(b) I_B = 25\mu\text{A}; R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{21\text{V} - 0.7\text{V}}{25\mu\text{A}} = 812\text{k}\Omega$$

$$(c) I_{CQ} \approx 3.4\text{mA}, V_{CEQ} \approx 10.75\text{V}$$

$$(d) \beta = \frac{I_C}{I_B} = \frac{3.4\text{mA}}{25\mu\text{A}} = 136$$

$$(e) \alpha = \frac{\beta}{\beta + 1} = \frac{136}{136 + 1} = \frac{136}{137} = 0.992$$

$$(f) I_{Csat} = \frac{V_{CC}}{R_C} = \frac{21\text{V}}{3\text{k}\Omega} = 7\text{mA}$$

(g) -

$$(h) P_D = V_{CEQ} I_{CQ} = (10.75\text{V})(3.4\text{mA}) = 36.55\text{mW}$$

$$(i) P_S = V_{CC} (I_C + I_B) = 21\text{V} (3.4\text{mA} + 25\mu\text{A}) = 71.92\text{mW}$$

$$(j) P_R = P_S - P_D = 71.92\text{mW} - 36.55\text{mW} = 35.37\text{mW}$$

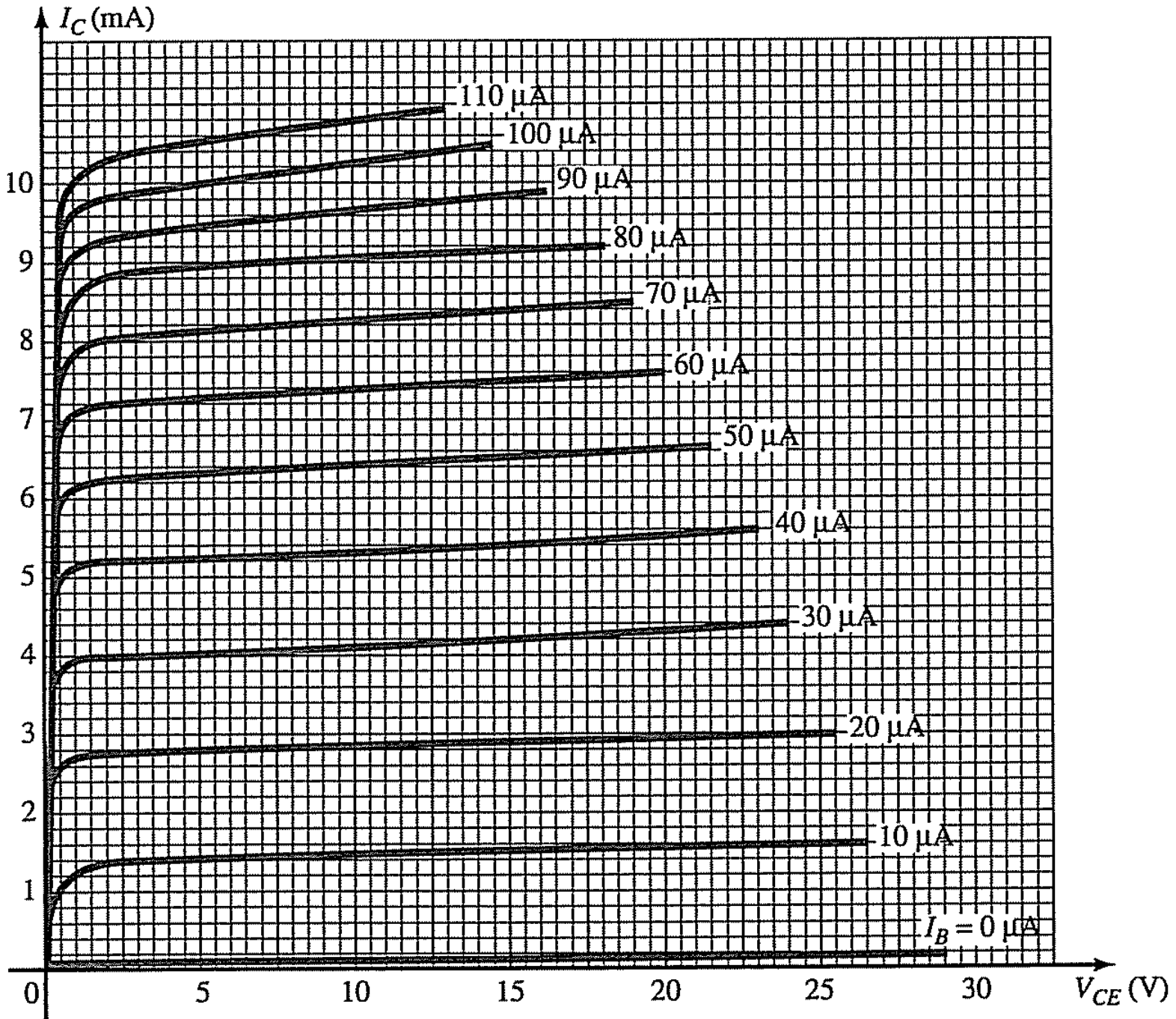


Figure 4.4 Problems 5.