


# LAB #05

## Objectives

1. To study the characteristics of Zener diode.
2. To study the voltage regulation in Zener diode regulation circuit.

## Theory

Zener diodes are used to maintain a fixed voltage. They are designed to 'breakdown' in a reliable and non-destructive way so that they can be used **in reverse** to maintain a fixed voltage across their terminals.

Example:   
a = anode, k = cathode


Circuit symbol:



The diagram shows how they are connected, with a resistor in series to limit the current. Zener diodes can be distinguished from ordinary diodes by their code and breakdown voltage which are printed on them. Zener diode codes begin BZX... or BZY... Their breakdown voltage is printed with V in place of a decimal point, so 4V7 means 4.7V for example.

Zener diodes are rated by their breakdown voltage and maximum power:

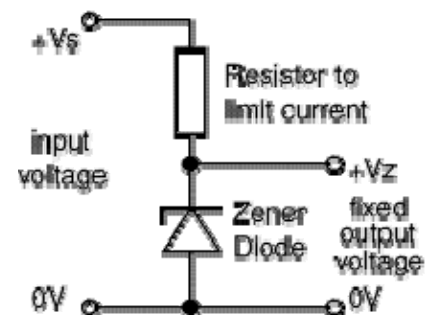- The minimum voltage available is 2.4V.
- Power ratings of 400mW and 1.3W are common.



## Preparatory Exercise

Q1) How does the way zener diodes are connected in a circuit differ from conventional diodes?

---



---



---



---

Q2) What is zener breakdown?

---



---

Q3) Mention any one application of zener diode.

---

---

---

Q4) What is the breakdown voltage of zener diode?

---

---

---

Q5) What is the basic principle of zener diode?

---

---

---

---

## **Requirement**

### **Instruments**

1. DC power supply
2. Function Generator
3. Digital Multimeter (DMM)

### **Components**

1. Diode : Zener (10-V)
2. Resistors:  $0.1\text{k}\Omega$ ,  $1\text{k}\Omega$ (2 pcs),  $3.3\text{k}\Omega$

## **Procedure**

### **Part A: Zener Diode Characteristics**

1. Construct the circuit of *Fig. 5.1*. Set the DC supply to 0 V and record the measured value of R.

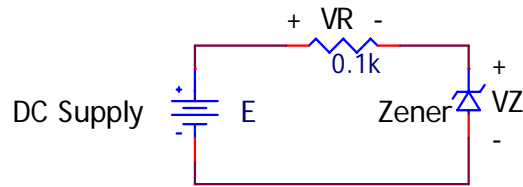


Fig. 5.1

2. Set the DC supply (E) to the values appearing in Table 5.1 and measure both  $V_Z$  and  $V_R$ . Calculate the Zener current,  $I_Z$  using the Ohm's law given in the table and complete the table.
3. Plot  $I_Z$  versus  $V_Z$  using the data in Table 5.1 on a graph paper.

### Part B: Zener Diode Regulation

1. Construct the circuit of Fig. 5.2. Record the measured value of each resistor.

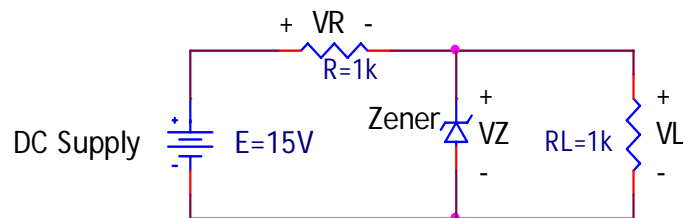


Fig. 5.2

2. Measure the value of  $V_L$  and  $V_R$ . Using the measured values, calculate the value for current across R,  $I_R$ , current across  $R_L$ ,  $I_L$ , and current across the zener diode,  $I_Z$ .
3. Change  $R_L$  to  $3.3\text{ k}\Omega$  and repeat Step 2.
4. Comment on the results obtained in Steps 2 and 3.

## Observation

### Results and Calculations

Part A: Zener Diode Characteristics

1. R (measured) = \_\_\_\_\_

2.

E (V)	0	1	3	5	7	9	11	13	15
$V_Z$ (V)									
$V_R$ (V)									
$I_Z = V_R / R_{\text{meas}}$ (mA)									

Table 5.1

## Part B: Zener Diode Regulation

1.  $R$  (measured) = \_\_\_\_\_,  $R_L$  (measured) = \_\_\_\_\_

2.  $V_R$  (measured) = \_\_\_\_\_,  $V_L$  (measured) = \_\_\_\_\_

$I_R = V_R / R =$  \_\_\_\_\_,  $I_L = V_L / R_L =$  \_\_\_\_\_,

$I_Z = I_R - I_L =$  \_\_\_\_\_

3. Change  $R_L$  to 3.3k $\Omega$ ;

$R_L$  (measured) = \_\_\_\_\_,

$V_R$  (measured) = \_\_\_\_\_,  $V_L$  (measured) = \_\_\_\_\_

$I_R = V_R / R =$  \_\_\_\_\_,  $I_L = V_L / R_L =$  \_\_\_\_\_,

$I_Z = I_R - I_L =$  \_\_\_\_\_