

EE-110 – Basic Electronics

Lecture #2

Diodes

Subtopics

1.0 Semiconductor diodes (3 hours)



- 1.1 Introduction to semiconductors materials
- 1.2 Introduction to diode
- 1.3 Introduction to Zener diode and LED

2.0 Diode applications (6 hours)

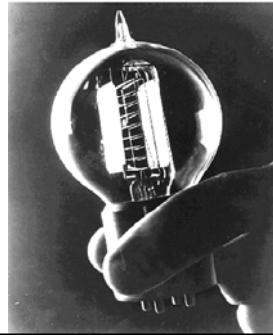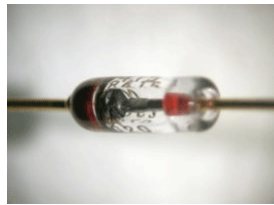- 2.1 Load line analysis and diode approximation
- 2.2 Series-Parallel Configuration
- 2.3 Half-wave and Full-wave rectification
- 2.4 Clippers and Clampers
- 2.5 Zener diode application


Early Diodes

- Thermionic diodes are thermionic valve devices (also known as vacuum tubes)
- Electrodes surrounded by a vacuum within a glass envelope, similar in appearance to incandescent light bulbs.



Semiconductor Diodes

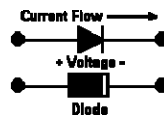- Most modern diodes are based on semiconductor p-n junctions
- In a p-n diode, conventional current can flow from the p-type side (the anode) to the n-type side (the cathode), but cannot flow in the opposite direction.




Diode symbol




Semiconductor Diodes

- Comparison of Ge, Si and GaAs diodes

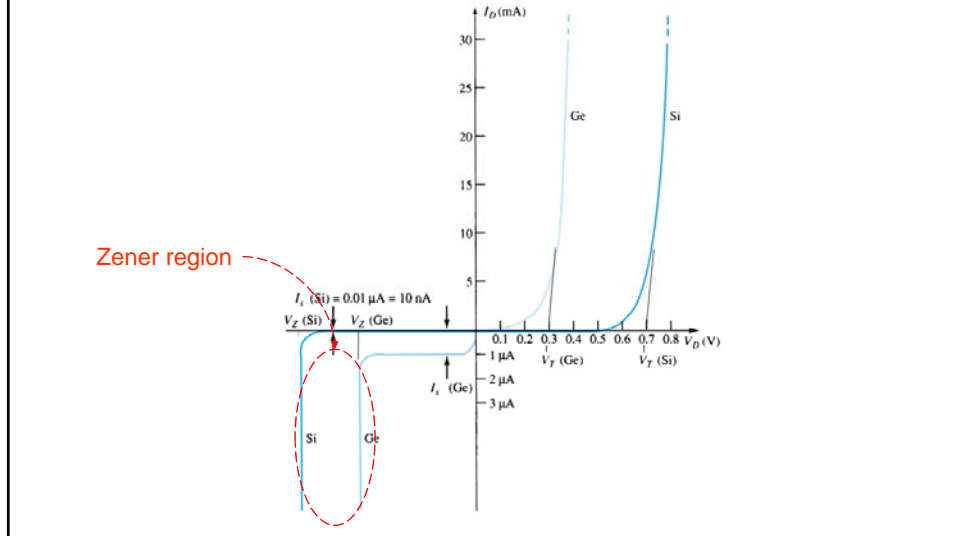

Zener Diode

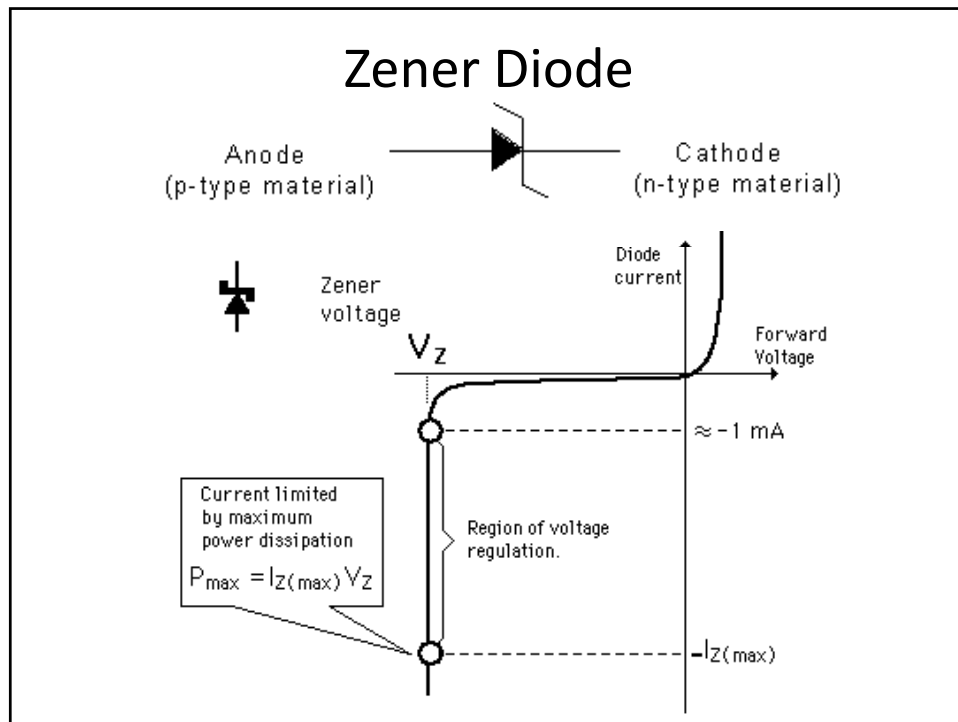- A special type of diode that is supposed to be reversed biased
- Zener diode works in zener region where the diode start to breakdown at breakdown avalanche voltage (V_Z), and the current is avalanche current (I_Z)
- It limits a voltage to a certain point to pass through the zener diode




LED (Light-Emitting Diode)

- In a forward-biased p-n junction, recombination of the holes and electrons requires energy possessed by the unbound free electrons
- In Si and Ge, most of the energy is dissipated in the form of heat and photons
- But in other material such as GaAs, the energy generate light but it is invisible for the eye to see (infrared)
- Other materials that emit light during forward-bias operation


LED (Light-Emitting Diode)

Color	Construction	Forward Voltage
Amber	AlInGaP	2.1
Blue	GaN	5.0
Green	GaP	2.2
Orange	GaAsP	2.0
Red	GaAsP	1.8
White	GaN	4.1
Yellow	AlInGaP	2.1

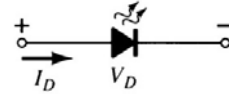

LED (Light-Emitting Diode)

- How an LED works

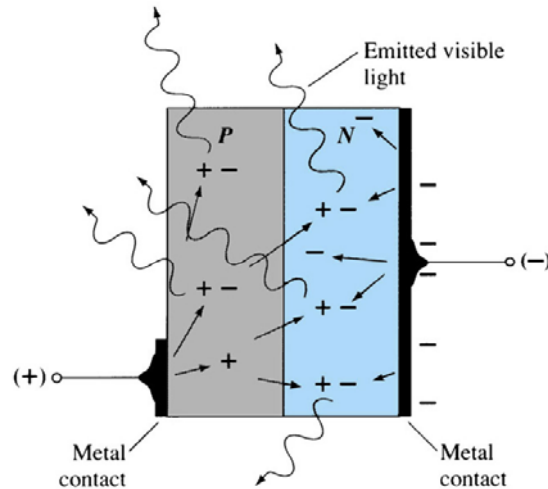


Diode Approximation

- Diode equivalent circuits:
 - Ideal Equivalent Circuit
 - Simplified Equivalent Circuit
 - Piecewise-Linear Equivalent Circuit
- Purpose: to represent diode


Piecewise-Linear Equivalent Circuit

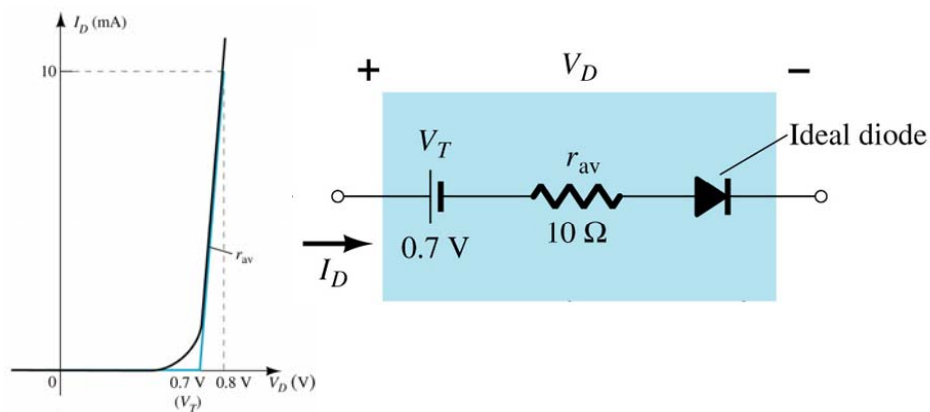- Approximation representation of the actual diode
- Diode have V_D and r_{av} for the slope region




Simplified Equivalent Circuit

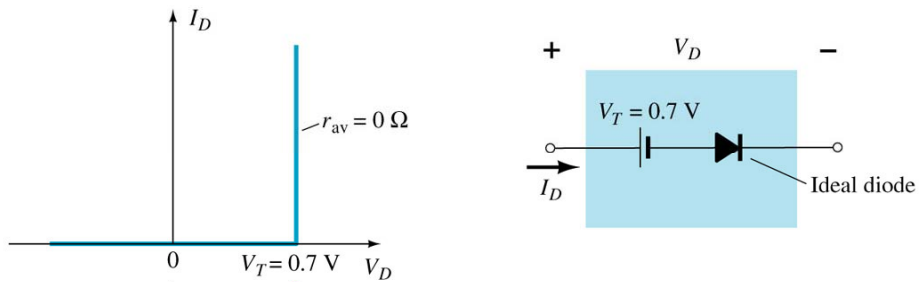- Assume straight vertical line of I_D at V_D
- No r_{av}




Ideal Equivalent Circuit

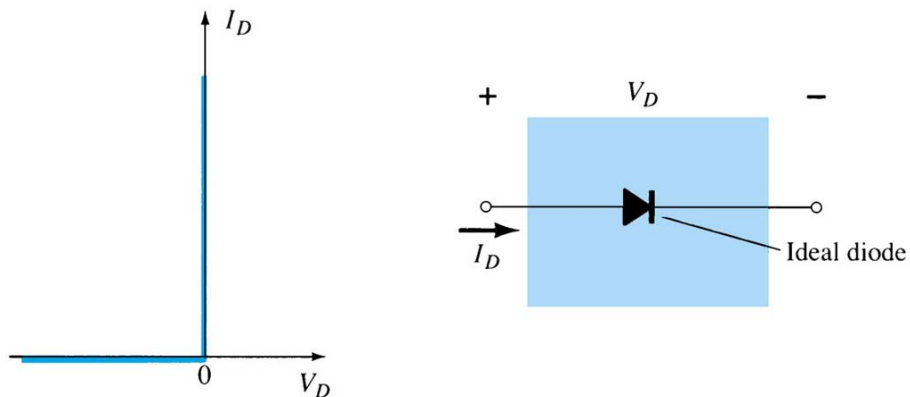- Diode as an ideal switch
- No V_D or r_{av}





Load-Line Analysis

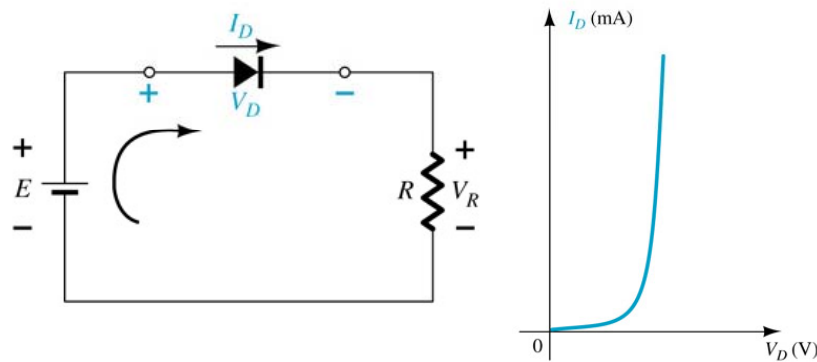- A simple analysis which used the diode characteristic to obtain the Q-point (operation point)
- A series diode circuit and characteristic:




Load-Line Analysis

- $E = V_D + V_R = V_D + I_D R$
- For $V_D = 0$, $E = 0 + I_D R = I_D R$, $\therefore I_D = E/R$
- For $I_D = 0$, $E = V_D + (0)R = V_D$, $\therefore V_D = E$
- Connect a line between E/R and E
- The overlap of the lines becomes the Q-point of the diode and I_{DQ} and V_{DQ} will be obtained

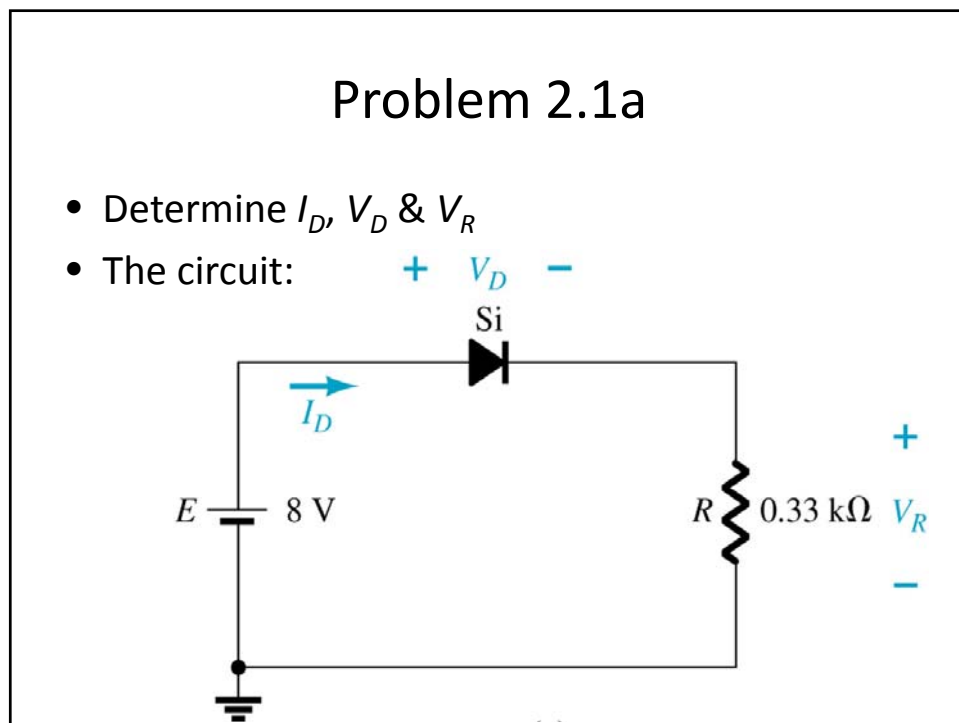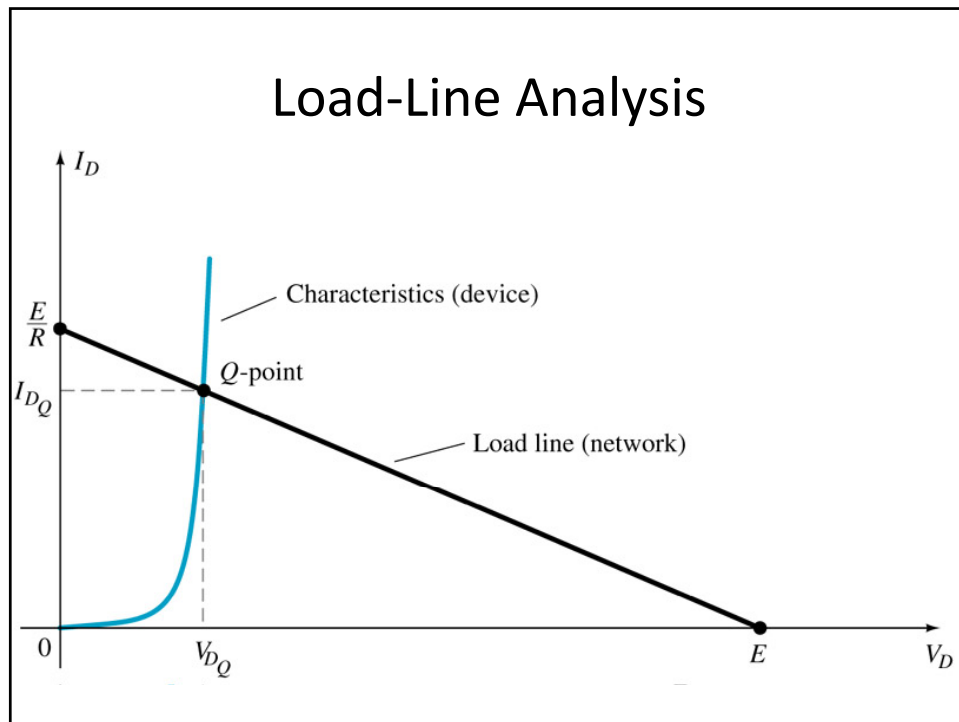

Problem 2.1a

- The diode characteristic:

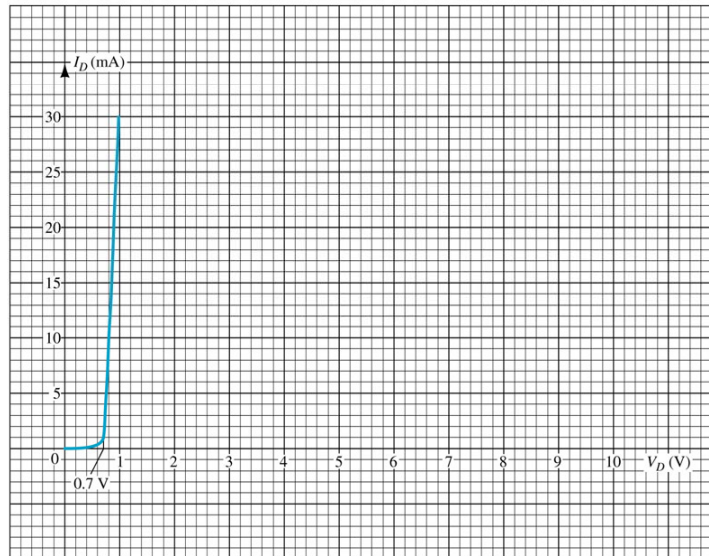

Problem 2.1a

- Solution:

– The circuit representation:

– For

$$E = V_D + V_R = V_D + I_D R$$

$$V_D = 0, \quad E = 0 + I_D R$$

$$\therefore I_D = E/R = 8/0.33k = 24.24 \text{ mA}$$


– For

$$I_D = 0, \quad E = V_D + (0)R$$

$$\therefore V_D = E = 8 \text{ V}$$

Problem 2.1a

- The load-line analysis becomes:

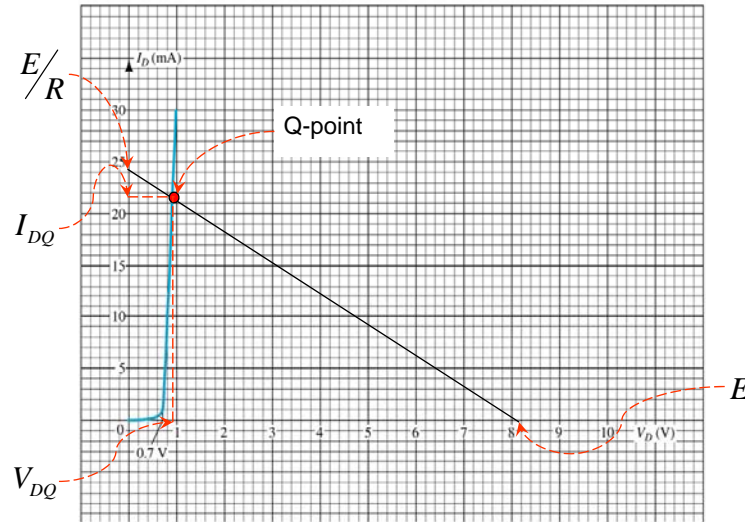

Problem 2.1a


- From the analysis:

- $V_{DQ} = V_D \approx 0.9$ V
- $I_{DQ} = I_D \approx 21.5$ mA
- For V_R

$$\begin{aligned} V_R &= I_D R \\ &= (21.5\text{m})(0.33\text{k}) \\ &= 7.095 \text{ V} \end{aligned}$$


Problem 2.1b

- Re-do Problem 2.1a using approximate (simplified) model for diode and compare the result
- The diode characteristic becomes:

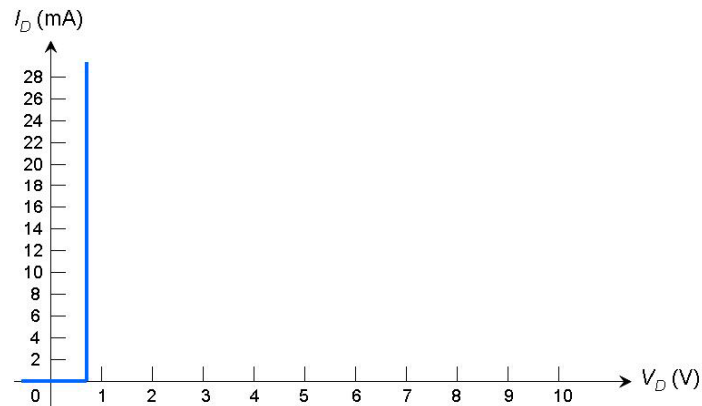

Problem 2.1b

- The solution:

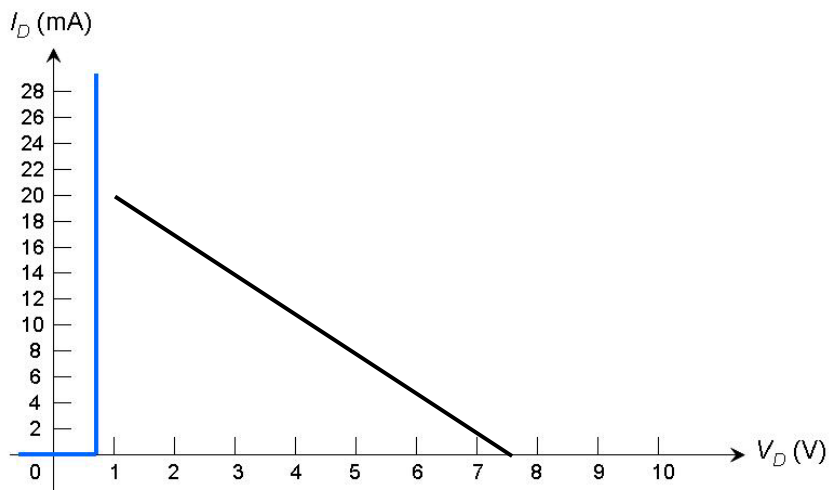

Problem 2.1b

- V_D is always 0.7 V, so $V_D = V_{DQ} = 0.7$ V
- From the graph, $I_{DQ} = I_D \approx 22$ mA
- So, we get $V_R = (22\text{m})(0.33\text{k}) = 7.26$ V ≈ 7.3 V
- Using Kirchoff's voltage law, $E = V_D + V_R$


$$8 = 0.7 + V_R$$

$$\therefore V_R = 7.3$$
 V

- The answer are the same


Problem 2.1c

- Re-do Problem 2.1a using ideal model for diode and compare the result
- The diode characteristic becomes:

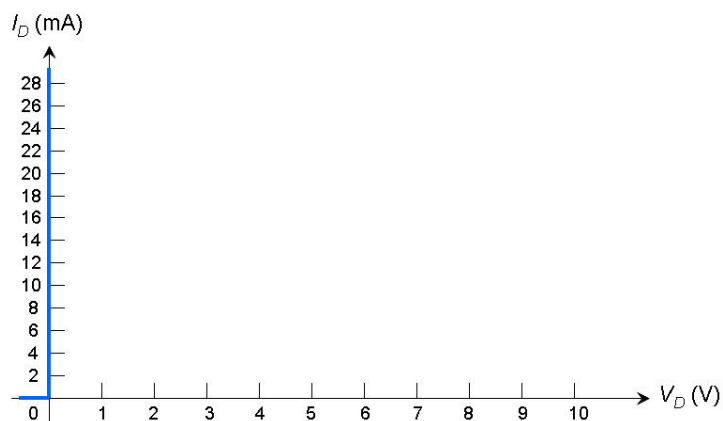

Problem 2.1c

- The solution

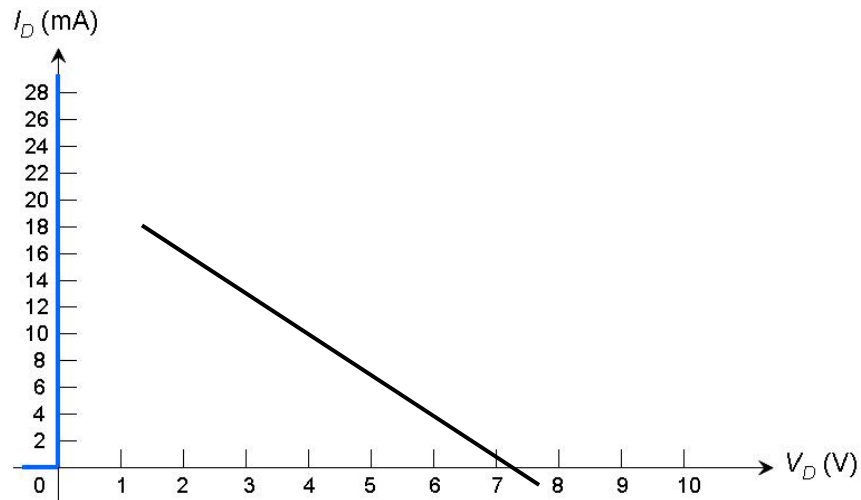

Problem 2.1c

- V_D is always 0 V, so $V_D = V_{DQ} = 0$ V
- It acts like an ideal switch
- From the graph, $I_{DQ} = I_D \approx 24.24$ mA
- So, we get $V_R = (24.24\text{m})(0.33\text{k}) = 7.9992$ V \approx 8 V
- Using Kirchoff's voltage law, $E = V_R$
- The answer are the same


$$\therefore V_R = 8 \text{ V}$$

Series-Parallel Configuration

- Diode can be applied to any circuits
- Usually diode is represented as an approximated (simplified) model diode
- To keep the calculation simple, just use the Kirchoff's voltage & current law
- Hint: it is easier to use nodal analysis technique for circuit representation
- Important: strong knowledge in CIRCUIT THEORY!!!!

Problem 2.5a

- Find I
- The circuit:

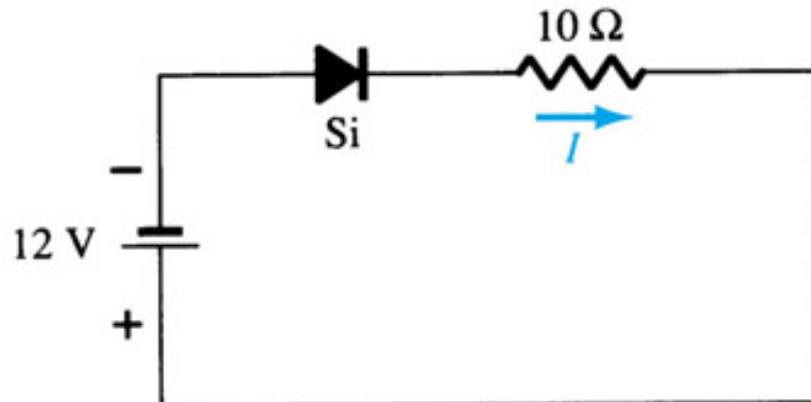


Problem 2.5a

- For Si, $V_D = 0.7 \text{ V}$
- Notice that the diode is in reverse-bias configuration
- So, no current will flow, $I = 0 \text{ A}$

Problem 2.5b


- Find I
- The circuit:

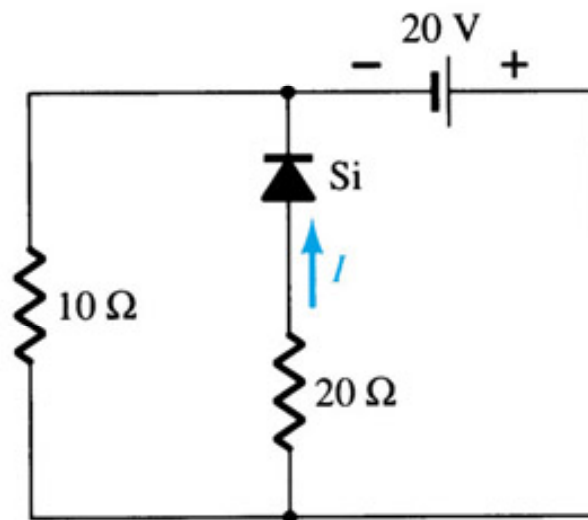

Problem 2.5b

Solution:

- Using nodal analysis, node V is equal to the voltage supplied, so $V = 20$

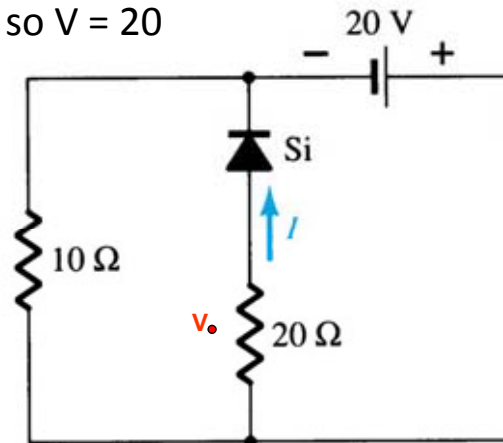


Problem 2.5b

- Using the simple Ohm's law:

$$I = \frac{V}{R} = \frac{20 - 0.7}{20} = 0.965 \text{ A}$$

Problem 2.5c


- Find I
- The circuit:

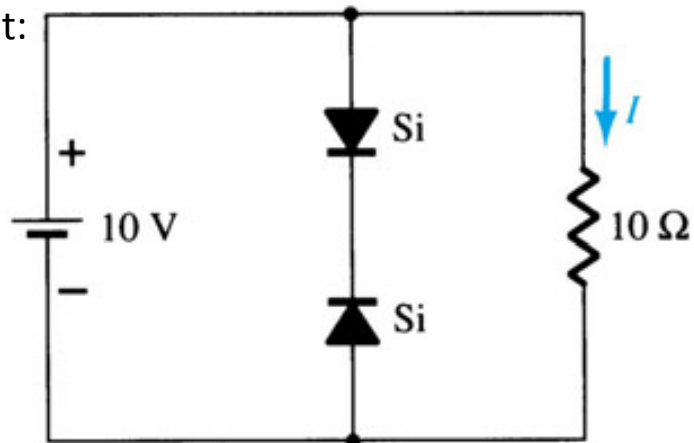

Problem 2.5c

Solution:

- One of the diode is in reverse-bias resulting in open circuit for that part

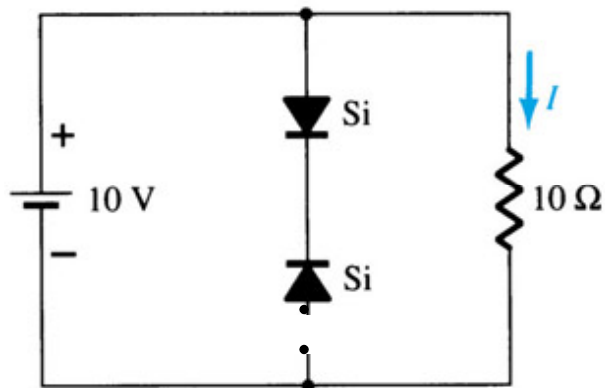


Problem 2.5c

- So, by using the simple Ohm's law:

$$I = \frac{V}{R} = \frac{10}{10} = 1 \text{ A}$$


Problem 2.7a

- Find V_o
- The circuit:

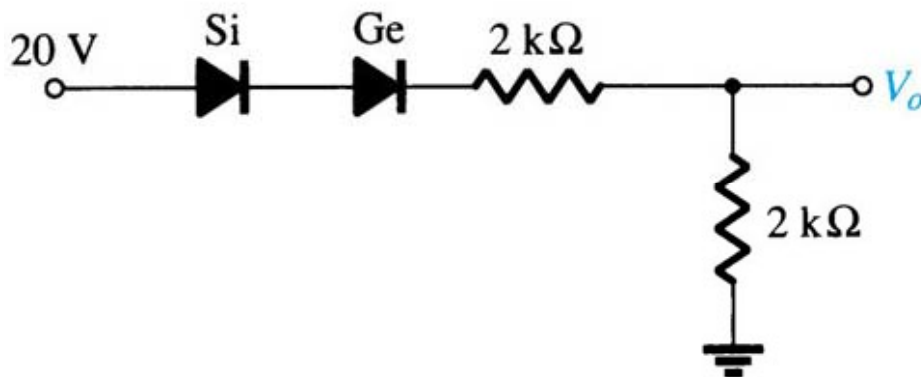

Problem 2.7a

- Both the diode are in forward-bias, so both are short-circuited
- For Si, $V_D = 0.7\text{ V}$
- For Ge, $V_D = 0.3\text{ V}$
- The circuit becomes:

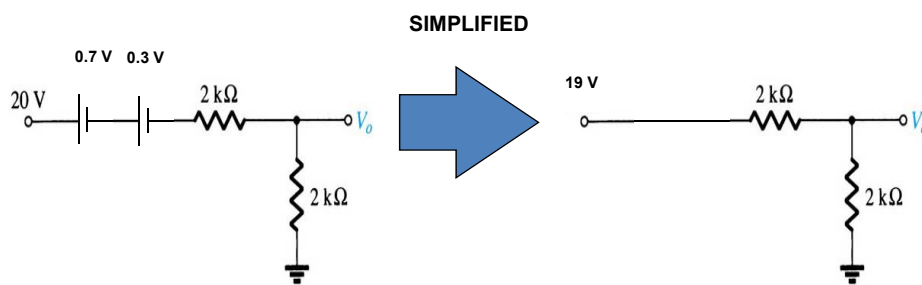

Problem 2.7a

Solution:


- Using nodal analysis, voltage at V_o :

$$\frac{19 - V_o}{2k} = \frac{V_o}{2k}$$

$$\therefore V_o = 9.5\text{ V}$$


Problem 2.7b

- Find V_o
- The circuit:

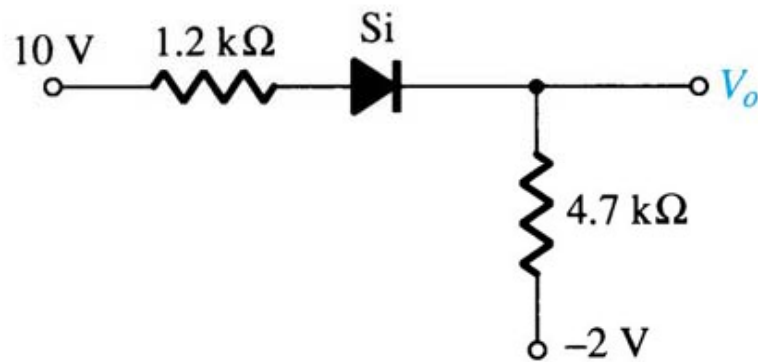

Problem 2.7b

- The circuit becomes:

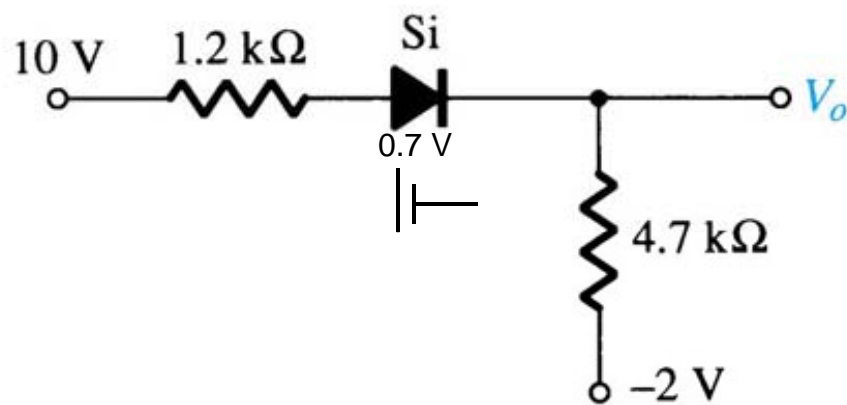

Problem 2.7b

Solution:


- The nodal analysis of node V_o :

$$\frac{10 - 0.7 - V_o}{1.2k} = \frac{V_o - (-2)}{4.7k}$$

$$\therefore V_o = 7 \text{ V}$$


Problem 2.11a

- Find V_o & I :
- The circuit:

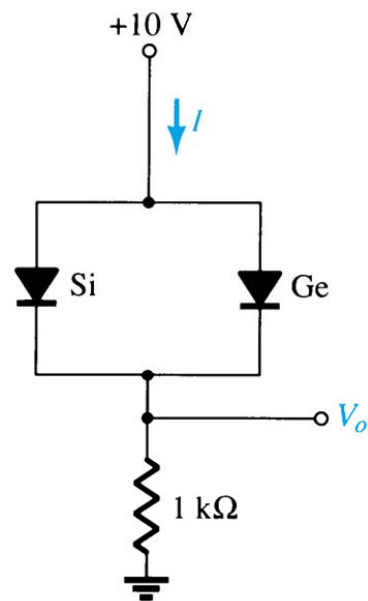

Problem 2.11a

- For Si, $V_D = 0.7 \text{ V}$
- For Ge, $V_D = 0.3 \text{ V}$
- Because of this, current will flow in the Ge's diode route
- Naturally, current will select the easiest/fastest route
- So, the circuit becomes:

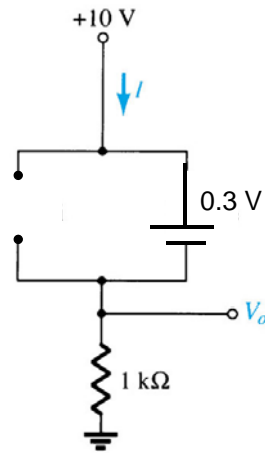

Problem 2.11a

Solution:

- Using Kirchoff's voltage law:


$$V_0 = 10 - 0.3 = 9.7 \text{ V}$$

- For I , by using basic Ohm's law:

$$I = \frac{V_0}{R} = \frac{9.7}{1k} = 9.7 \text{ mA}$$


Problem 2.11b

- Find V_o & I :
- The circuit:

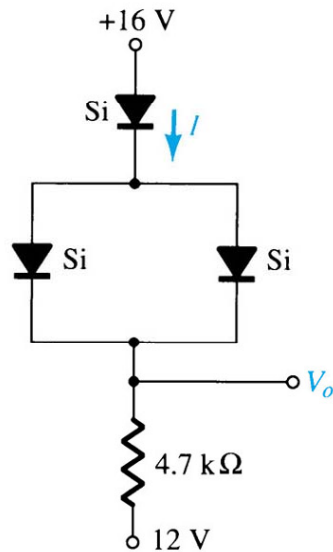

Problem 2.11b

- For the same type of diode, the circuit will become:
- Because there is no resistor exist in the parallel route of the diode, current will flow in only one of the diode's route

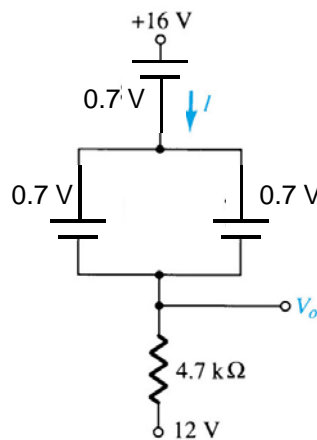

Problem 2.11b

Solution:

- Using Kirchoff's voltage law:


$$V_o = 16 - 0.7 - 0.7 = 14.6 \text{ V}$$

- For I , by using Ohm's law:

$$I = \frac{14.6 - 12}{4.7k} = 0.553 \text{ mA}$$


Problem 2.13

- Find V_o & I_D
- The circuit:

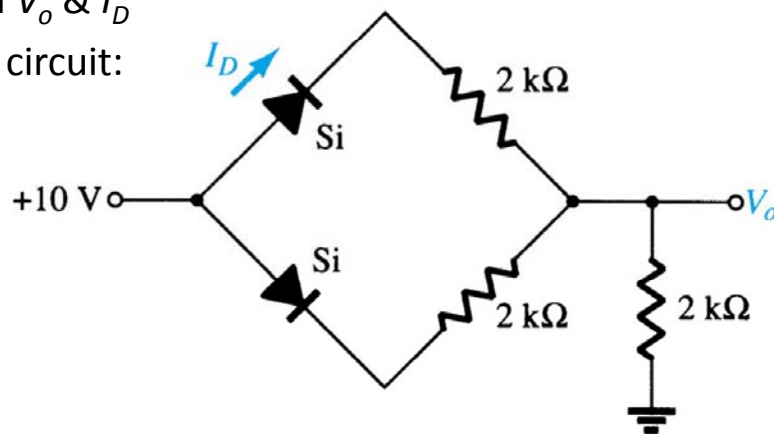

Problem 2.13

- The circuit becomes:

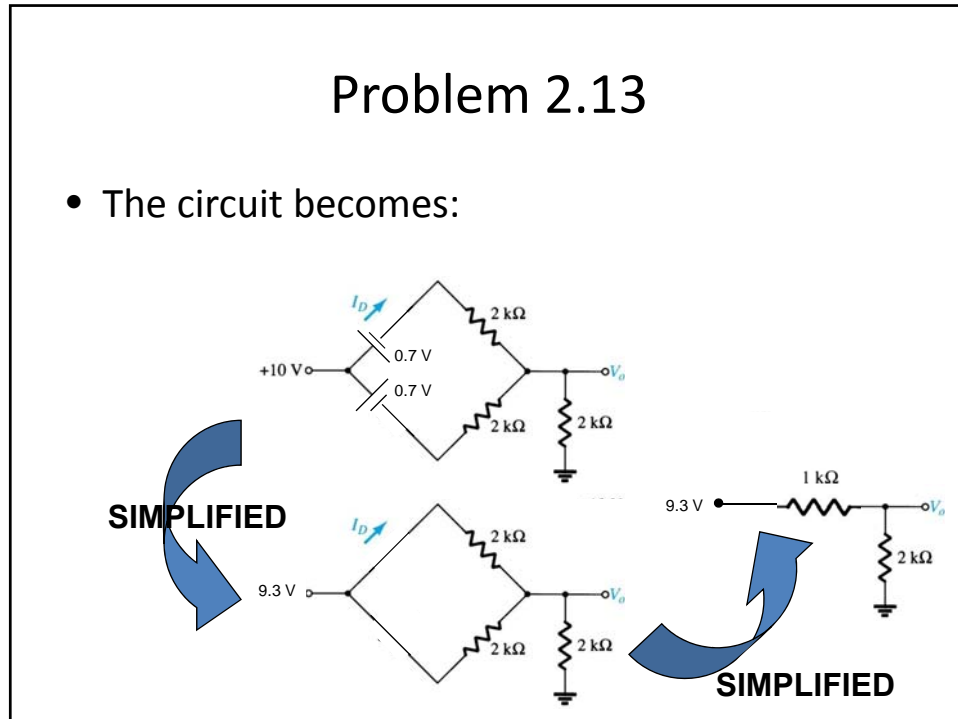

Problem 2.13

Solution:

- The nodal analysis for node V_o :

$$\frac{9.3 - V_o}{1k} = \frac{V_o}{2k}$$

$$\therefore V_o = 6.2 \text{ V}$$


- For I_D :
$$I_D = \frac{9.3 - 6.2}{2k} = 1.55 \text{ mA}$$

Rectification

- Rectify means improvement, cure healing (pembaikan, penambahbaikan)
- For a sinusoidal waveform or any supply that has a variation of input value, diode can be used for rectification
- Rectification are used to modified the input value to become only the signal that we want


Half-Wave Rectification

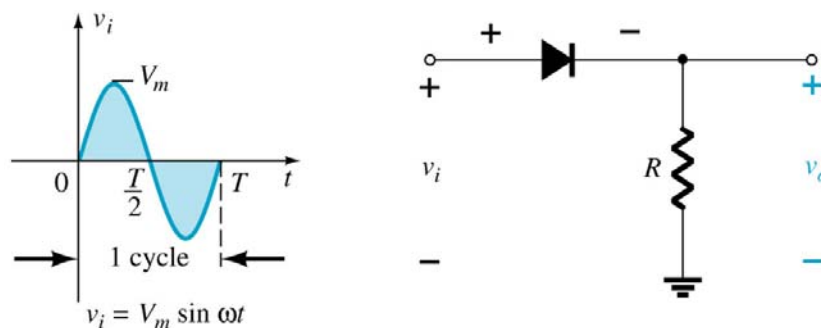- For a full cycle of a sinusoidal or continuous waveform, only half of the waveform is taken to be rectified




Half-Wave Rectification

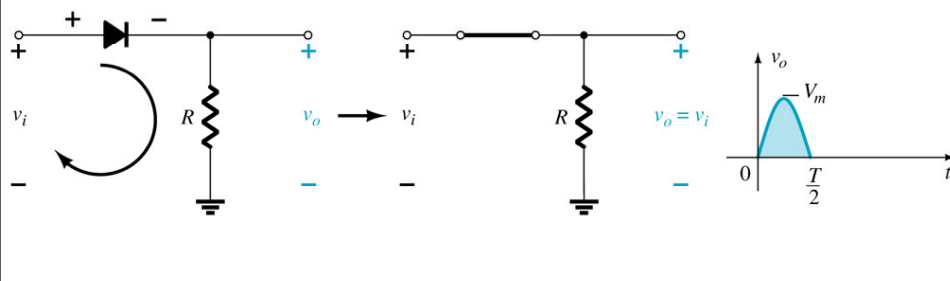- For the period $0 \rightarrow T/2$, the sinusoidal input will give a forward bias supply to the circuit
- The diode will “on” and current will pass through
- Assume that the diode is ideal




Half-Wave Rectification

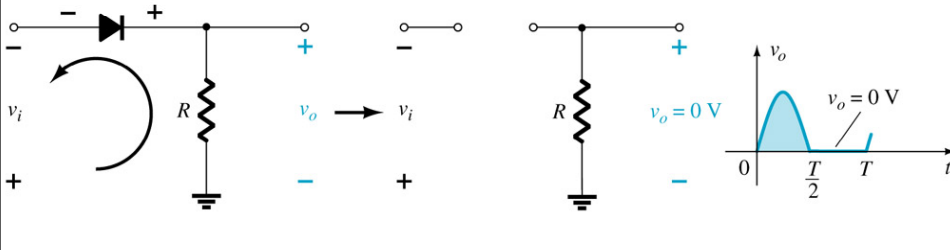- For the period $T/2 \rightarrow T$, the sinusoidal input will give a reverse bias supply to the circuit
- The diode will “off” and no current can pass through
- Assume that the diode is ideal



Half-Wave Rectification

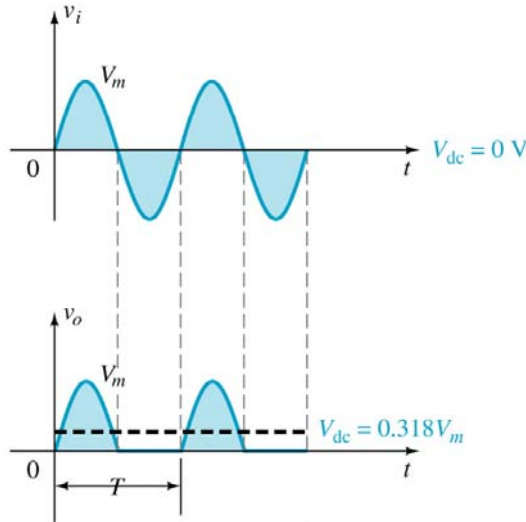- For a continuous periodic waveform, the rectified waveform will become:




- Where as:

$$V_{dc} = 0.318V_m$$

Problem 2.25

- Sketch V_o and determine V_{dc} :

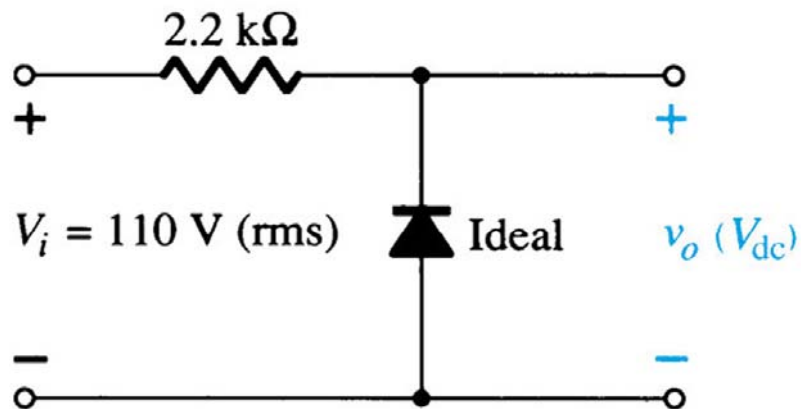


Problem 2.25

Solution:

- To obtain V_m from V_{rms} :

$$\begin{aligned} V_m &= \sqrt{2}V_{rms} \\ &= \sqrt{2}(110) = 155.56 \text{ V} \end{aligned}$$



- The output V_o will be:

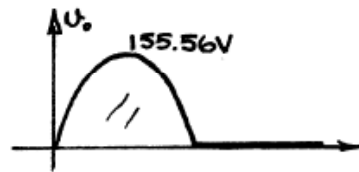

- V_{dc} will be: $V_{dc} = 0.318V_m$
 $= 0.318(155.56) = 49.47 \text{ V}$



Problem 2.26

- Sketch V_o

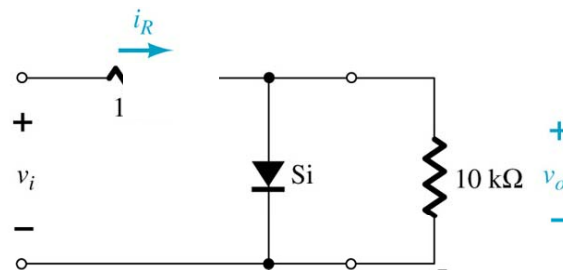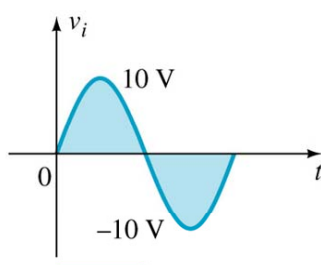


Problem 2.26

- Solution:
- For the positive input supply:
- The circuit becomes:
- For $V_i < 0.7V$:
- For $V_i \geq 0.7V$:

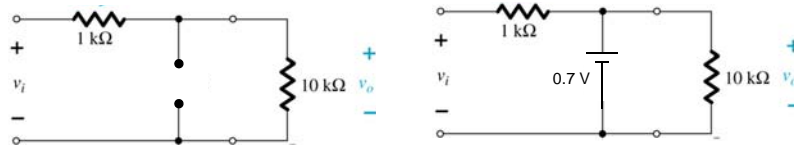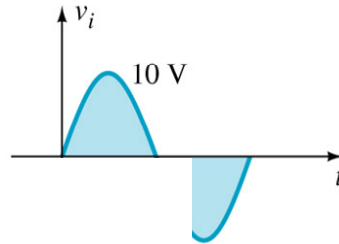

Problem 2.26

- The output for the positive input supply becomes:
- For the negative input supply:

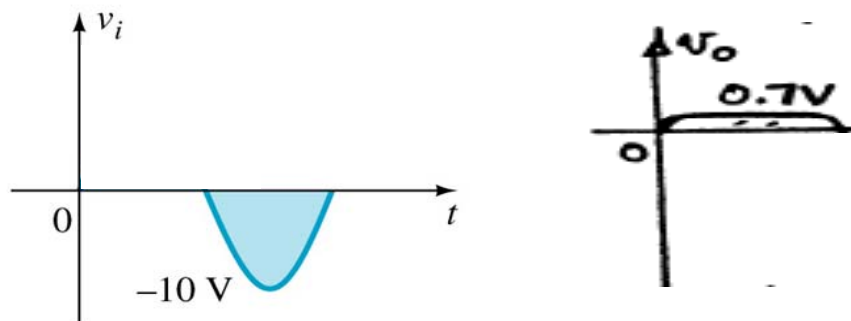


Problem 2.26

- The circuit becomes:
- For maximum V_o : The output becomes:


$$\frac{-10 - V_o}{1k} = \frac{V_o}{10k}$$

$$\therefore V_o = -9.091V$$

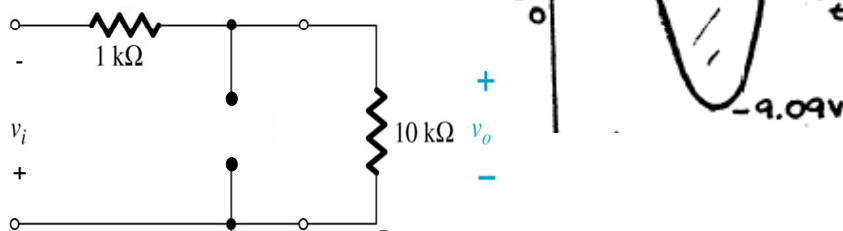

Problem 2.26

- Combine both the output becomes:

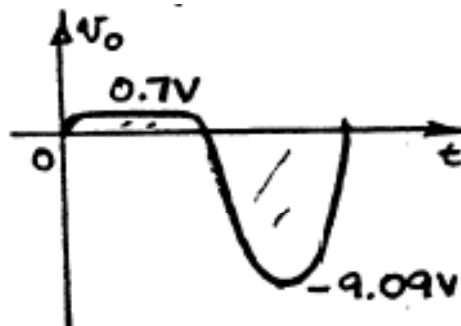

PIV or PRV

- Peak Inverse Voltage (PIV) or Peak Reverse Voltage (PRV)
- It is a rating to make sure for the reverse-bias operation, the diode didn't enter the Zener region
- PIV is set according to the circuit and the input voltage

$$\boxed{\text{PIV rating} \geq V_m} \text{ for half-wave rectifier}$$


Full-Wave Rectification

- The whole cycle of input signal is used and rectified
- Two commonly types of full-wave rectifier:
 - Bridge Network
 - Center-Tapped (CT) Transformer
- The dc level from a sinusoidal input can be improved 100%. So the V_{dc} becomes:

$$\boxed{V_{dc} = 0.636V_m}$$


Full-Wave Rectifier: Bridge Network

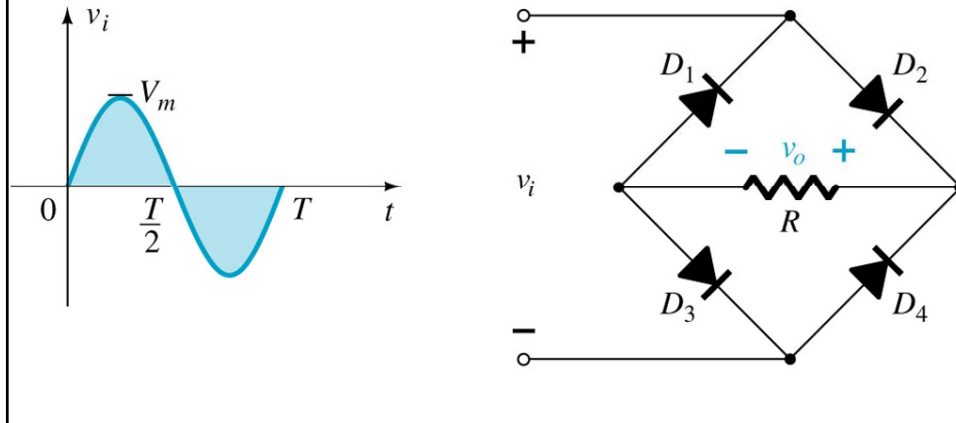- The most commonly bridge network configuration are build with 4 diodes




Full-Wave Rectifier: Bridge Network

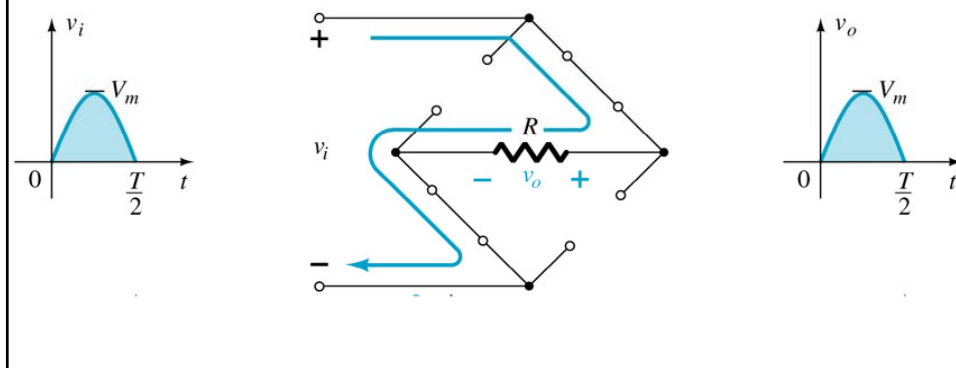- For the positive input supply, the current will take the route as shown below, and the output will becomes:




Full-Wave Rectifier: Bridge Network

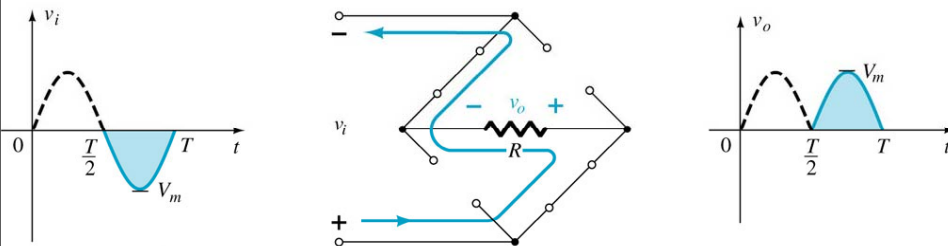- For the negative input supply, the current will take the route as shown below, and the output will becomes:



Full-Wave Rectifier: Bridge Network

- Combine both of the output becomes:

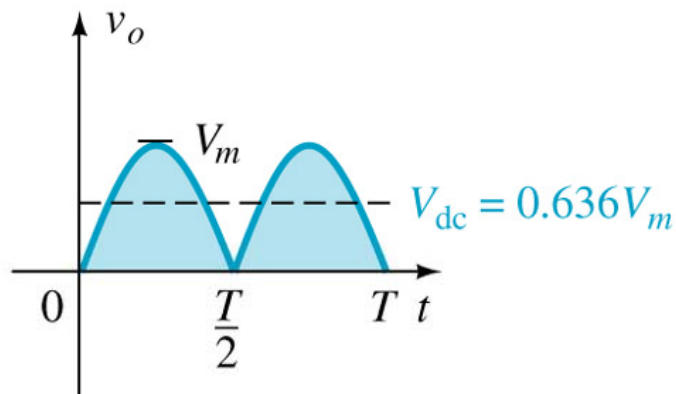

Full-Wave Rectifier: Bridge Network


- Due to the maximum voltage from the input supply is V_m , to keep the diode away from the Zener region, the PIV rating is:

$$\text{PIV rating} \geq V_m$$

for full-wave rectifier: bridge network


Full-Wave Rectifier: Center-Tapped (CT) Transformer

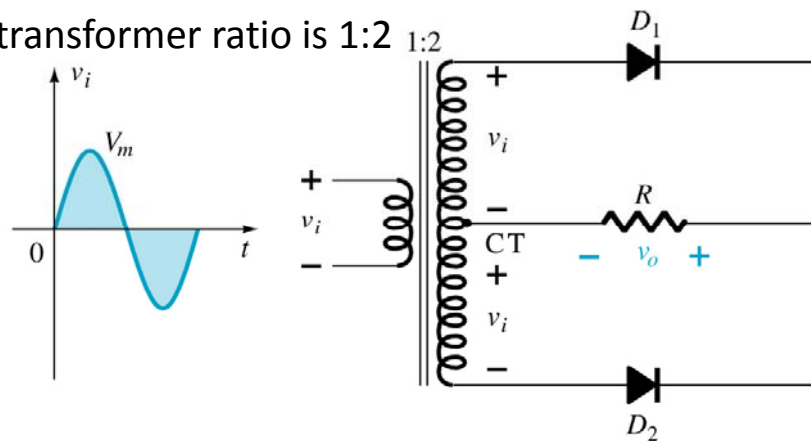- It is constructed with 2 diodes and a center-tapped transformer
- The transformer ratio is 1:2




Full-Wave Rectifier: Center-Tapped (CT) Transformer

- For the positive input supply:

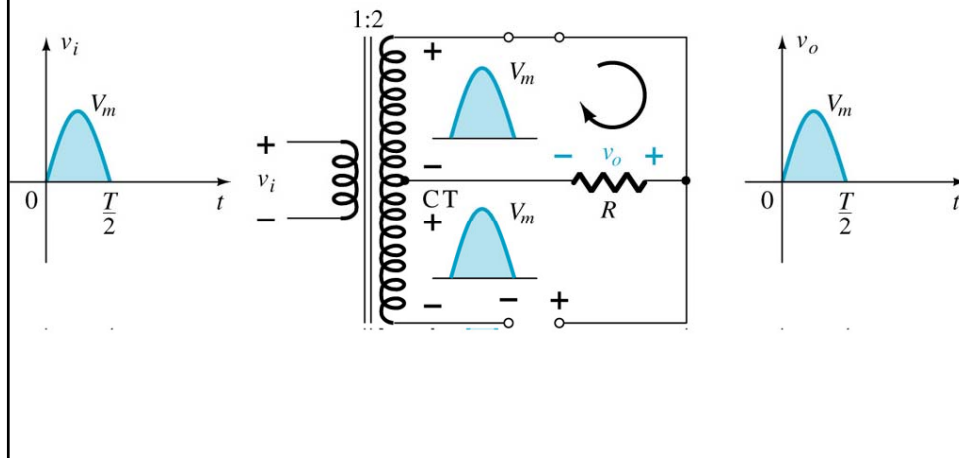

Full-Wave Rectifier: Center-Tapped (CT) Transformer

- For the negative input supply:

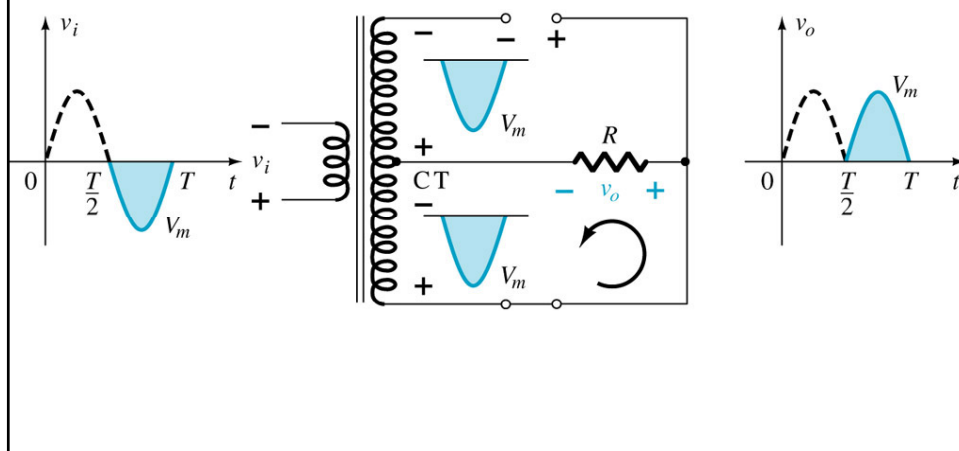

Problem 2.28

- The circuit:

