

EE-110 – Basic Electronics

Bipolar Junction Transistor (BJT)

- Introduction

Subtopics

3.0 Bipolar Junction Transistors (6 Hours)

3.1 Transistor construction and operation

3.2 Transistor configuration



3.3 Transistor datasheet and terminal identification

Introduction

- Bipolar means there are two polarities involve in this transistor when operating
- The polarities are the carries involve in the operation of the transistor: holes and electrons
- If only one carrier is employed (holes or electrons), it is said to be unipolar (ex: Diode)

Introduction

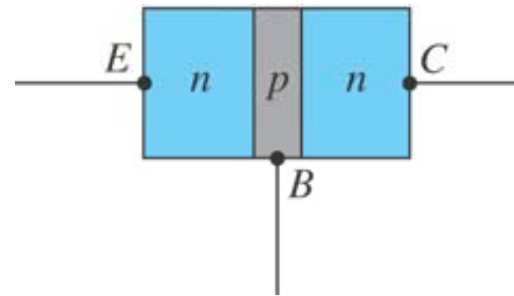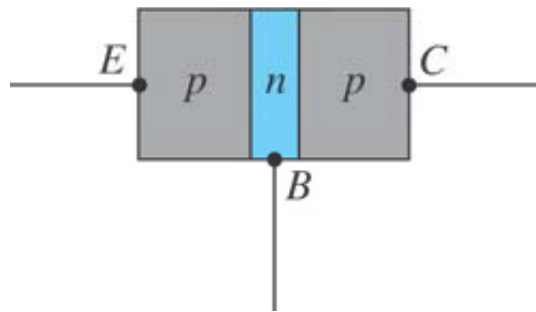- BJT is a three-layer semiconductor
- Two types of BJT
 - pnp:
 - npn:



– E = emitter, B = base, C = collector

Transistor Construction

- Layer width:
 - outer layer \gg inner layer
- Doping:
 - emitter layer is highly doped (more conductivity)
 - collector layer is lightly doped (less conductivity)
 - base layer is more lightly doped (lesser conductivity)
 - doping: $E > C > B$

Transistor Operation


- The operation of pnp and npn are the same except for the current flow
 - For pnp:
 - Current flow from E to B and C
 - For npn:
 - Current flow from B and C to E
- As for that, both type will have the current equation:

$$I_E = I_B + I_C$$


Transistor Operation

- Proper biasing for pnp and npn transistor:

– pnp

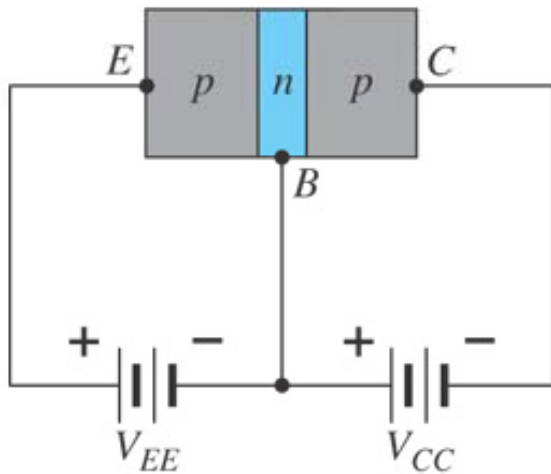


- npn

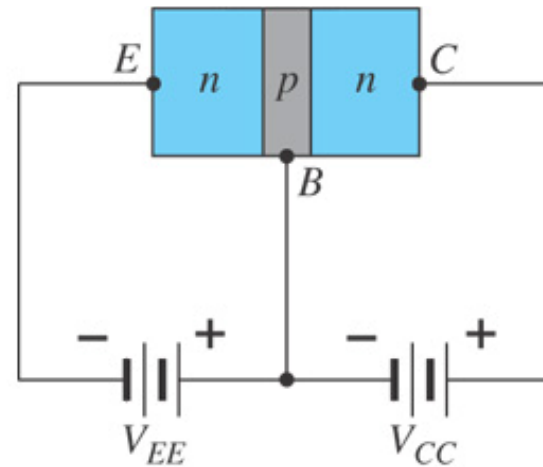

– This proper biasing is for transistor operation in active region (will be discussed in DC biasing)

Transistor Operation

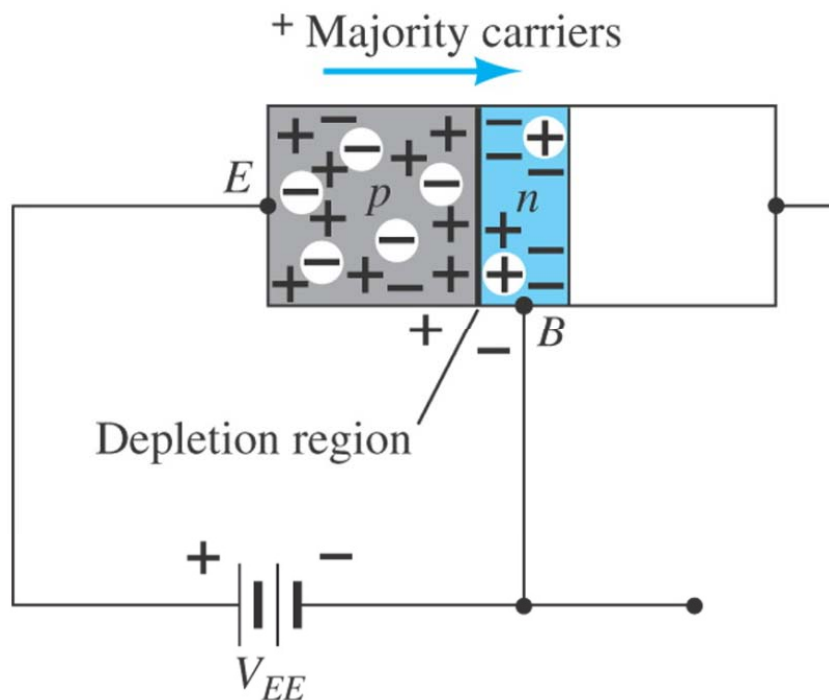
- Examine the pnp transistor for its forward biased junction at terminal E to B:



- It is very similar to a forward-biased diode
- Majority carrier (holes) flows from E to B
- Minority carrier (electrons) flows from B to E
- Resulting in small depletion region
- This means that the current flows heavily from E to B

Transistor Operation

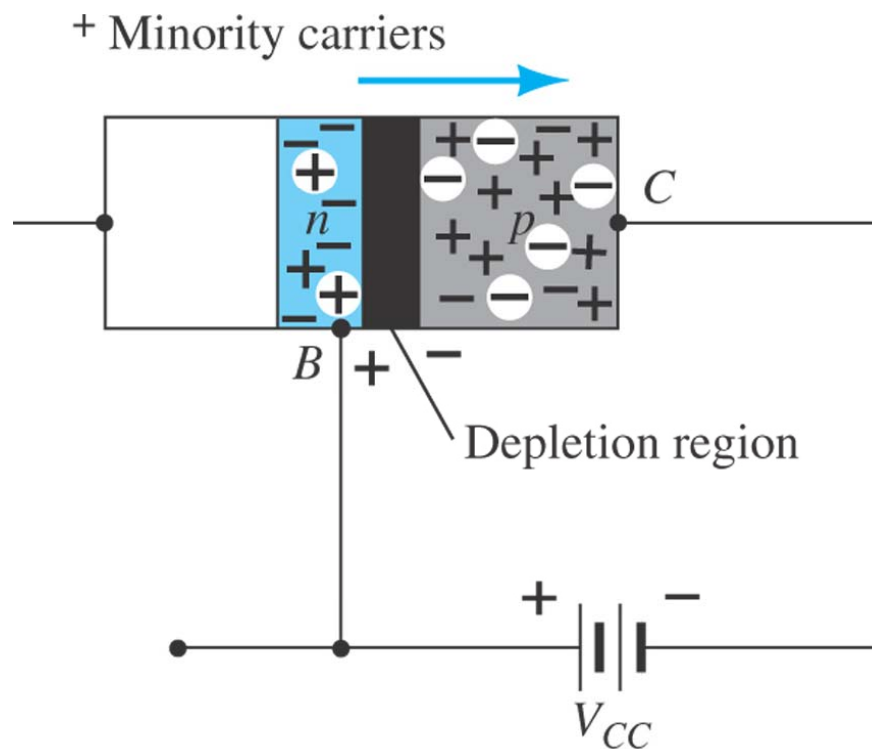
- Next, examine its reverse biased junction at terminal B to C:



- It is very similar to a reverse-biased diode
- Only minority carrier (holes) flows from B to C
- There are no majority carrier flows
- Resulting in big depletion region
- This means that the current flows lightly from E to B

Transistor Operation

- Combine both operation discussed:

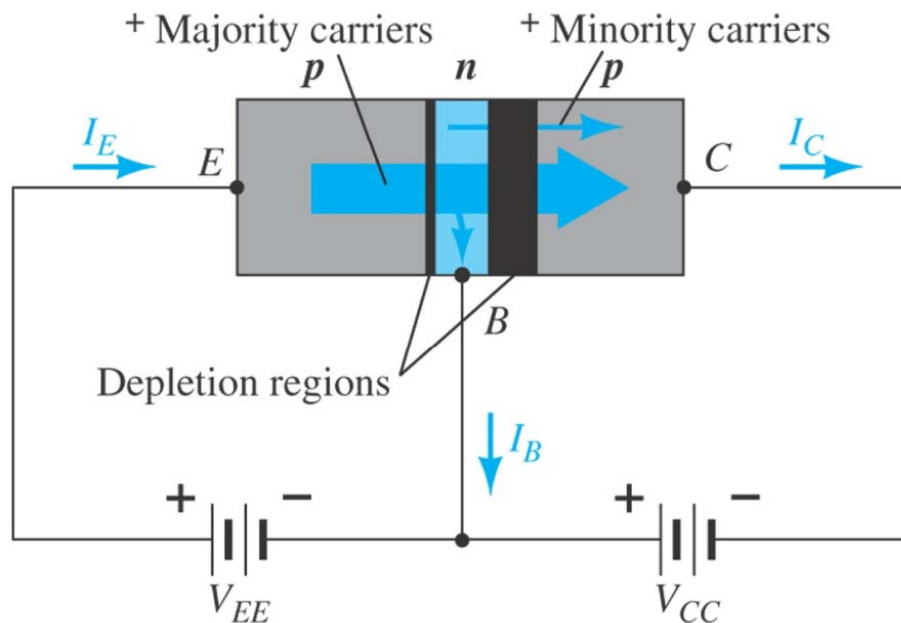



- Despite of big depletion region at B-C, but the majority carriers along with minority carriers will flow through region C, resulting in $I_E \approx I_C$ (usually in milliamperes)
- Very few minority carrier will flow to terminal B due to the minority carrier, resulting in I_B in only a few microamperes
- For npn transistor, all the discussion above are reversed, by mean the current flows

Transistor Configuration

- There are three commonly used configuration in BJT
 - Common-base (CB) configuration
 - Common-emitter (CE) configuration
 - Common-collector (CC) configuration
- Further on, these configuration will be discussed on npn transistor first, the pnp transistor is the exact reverse (in means of current flows) of the npn transistor


CB Configuration

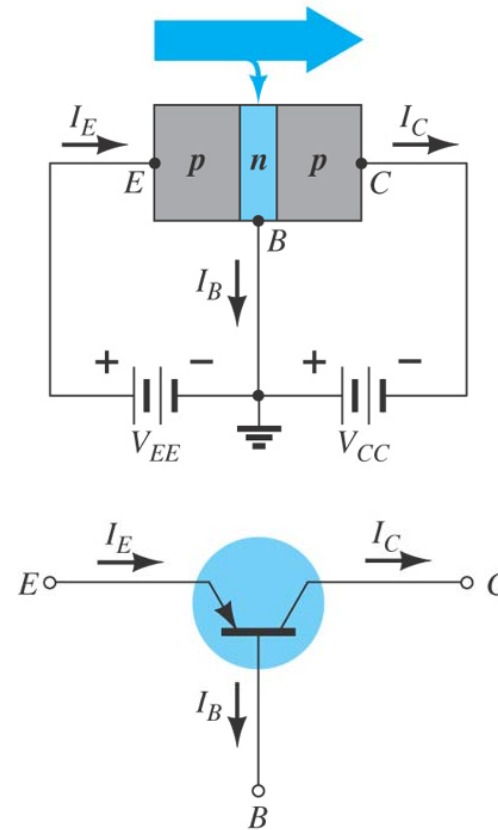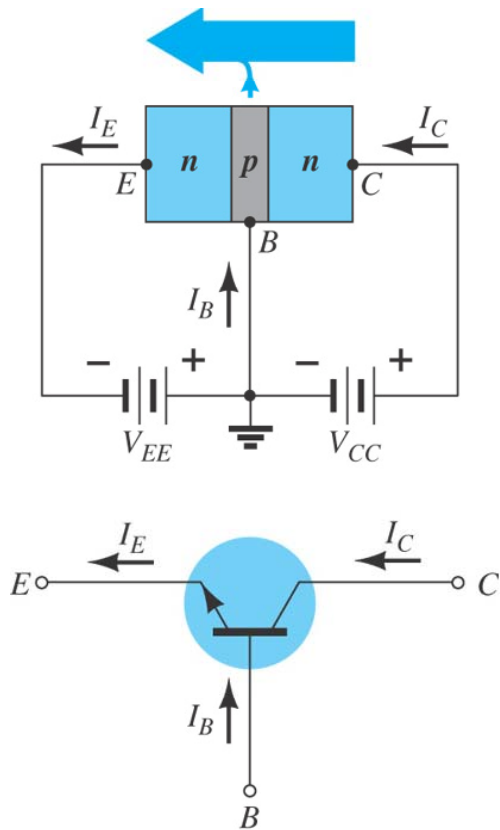- By applying the proper biasing and grounding the base terminal:




CB Configuration

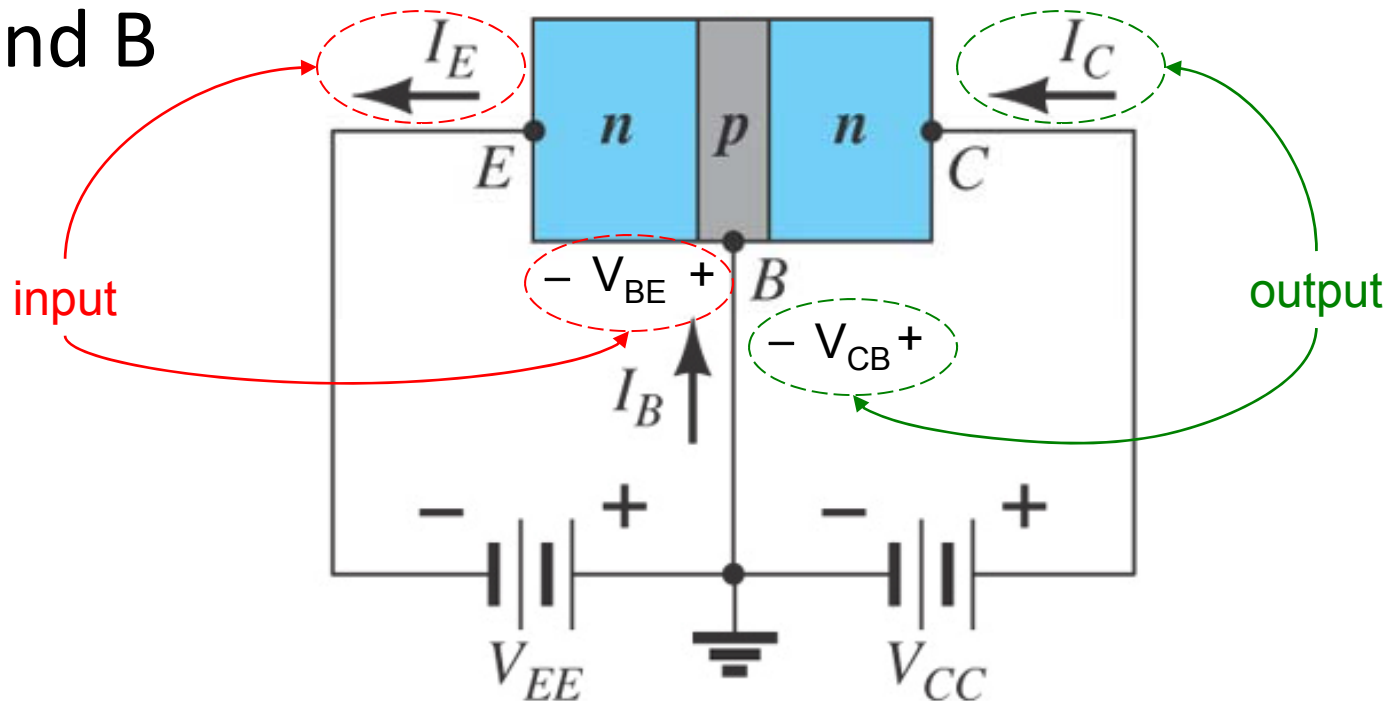- In CB configuration, the input terminal is between terminal E and B (due to ground at B)
- The output terminal is fixed between terminal C and B




CB Configuration

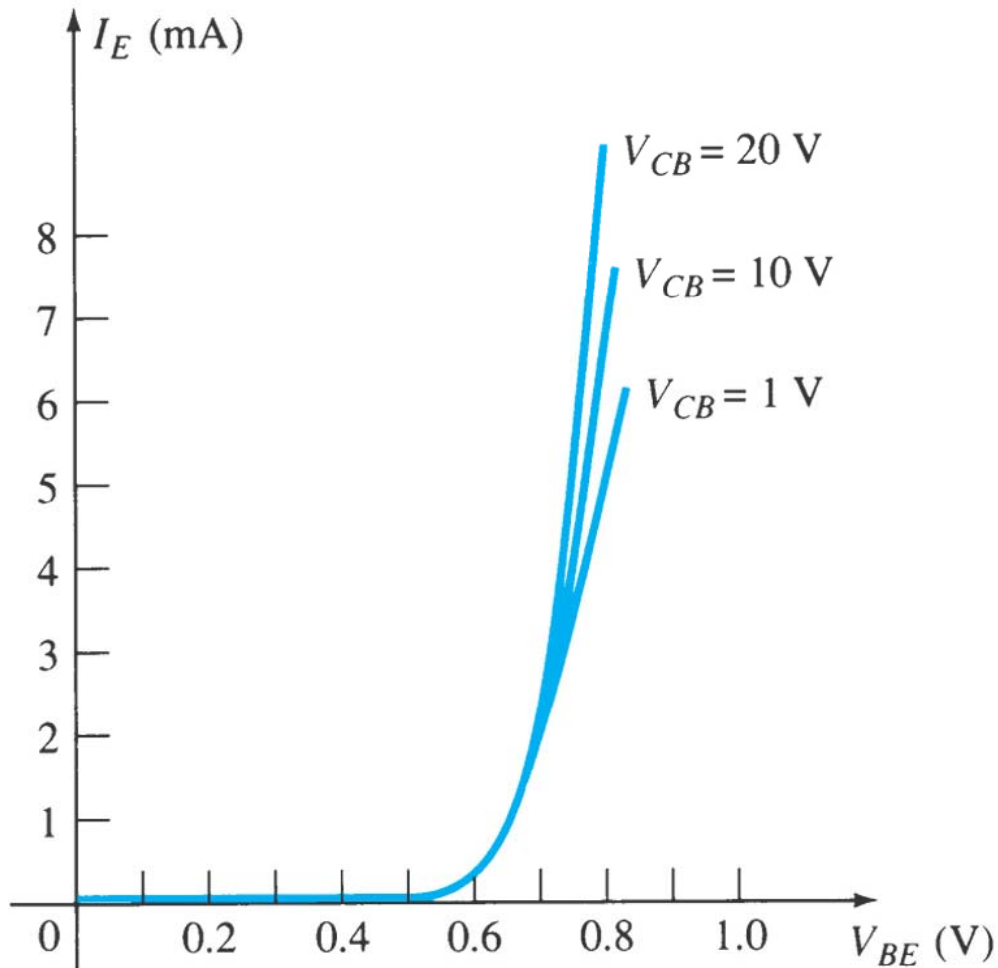

- By examining the input, plotting the V_{BE} and I_E , the output V_{CB} is fixed at $V_{BE} \approx 0.7$ V
- Despite the increasing of output voltage, the input voltage remains the same
- Recall back for semiconductor diode in forward-biased, the voltage is 0.7
- BJT used the same material as in diode

CB Configuration

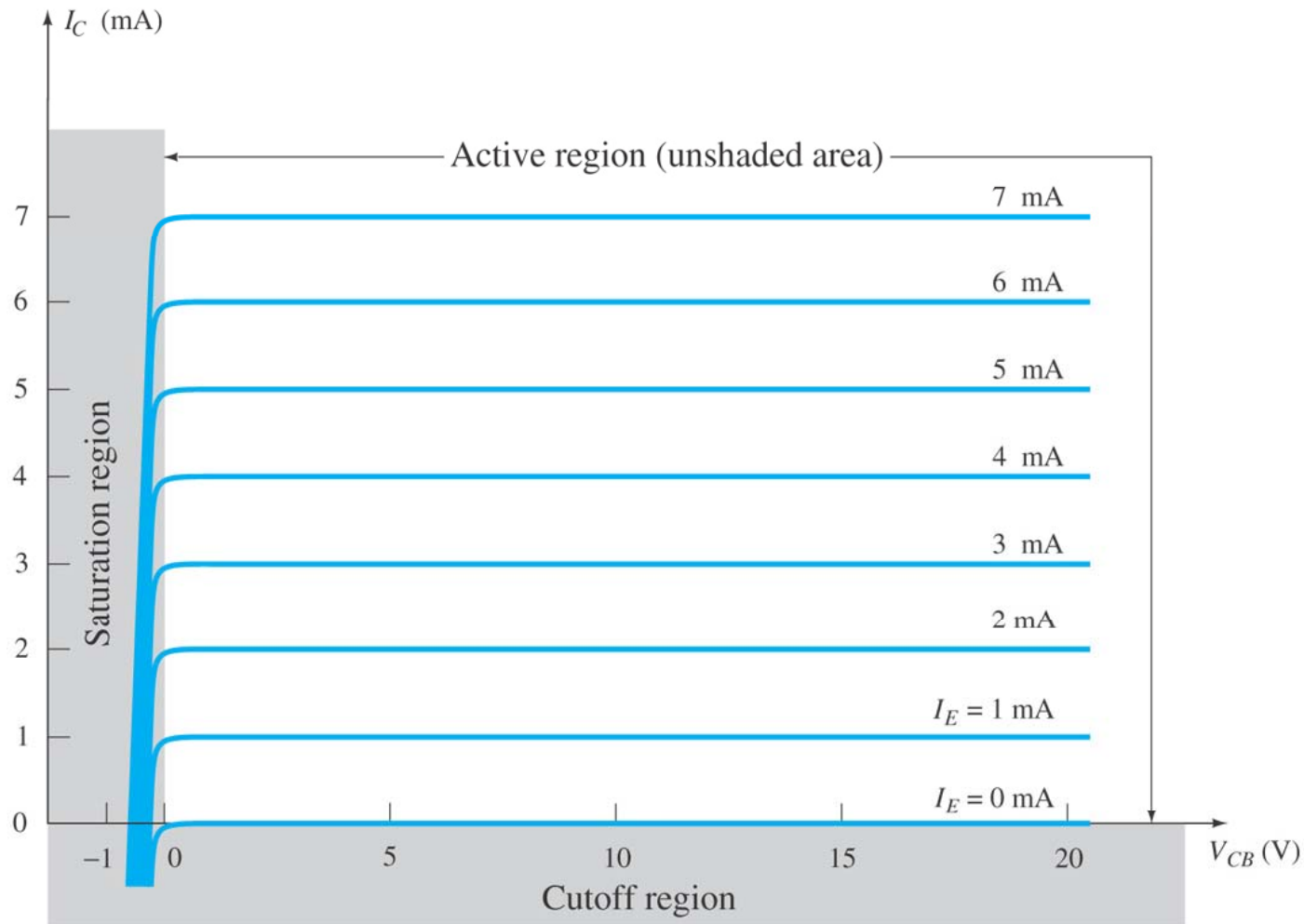- Examine the output at terminal C and B:



CB Configuration

- There are 3 region of operation:
 - Active region
 - Cutoff region
 - Saturation region
- In active region, there's a relation between I_E and I_C (this is only approximation):

$$I_E \cong I_C$$

CB Configuration

- In cutoff region, output (collector) current is zero (open-circuit equivalent):

$$I_C = 0 \text{ A}$$

- In saturation region, output (collector-base) voltage is zero (short-circuit equivalent):

$$V_{CB} = 0 \text{ V}$$

Alpha (α)

- By assuming $I_E = I_C$, it is assumed that $I_B = 0$, even though I_B is in microamperes (this is only approximation)
- For the exact value ($I_B \neq 0$), the emitter and collector current will be:


$$I_C = \alpha I_E$$

- The value of α is below 1 but near 1 (range 0.90 to 0.998)

Problem 3.13

- Question:
 - By using the characteristic given,
 - a) Determine the collector current if $I_E = 4.5 \text{ mA}$ and $V_{CB} = 4 \text{ V}$
 - b) Determine the collector current if $I_E = 4.5 \text{ mA}$ and $V_{CB} = 16 \text{ V}$
 - c) How have the change in V_{CB} affected the resulting level of I_C
 - d) On an approximate basis, how are I_E and I_C related?

Problem 3.13

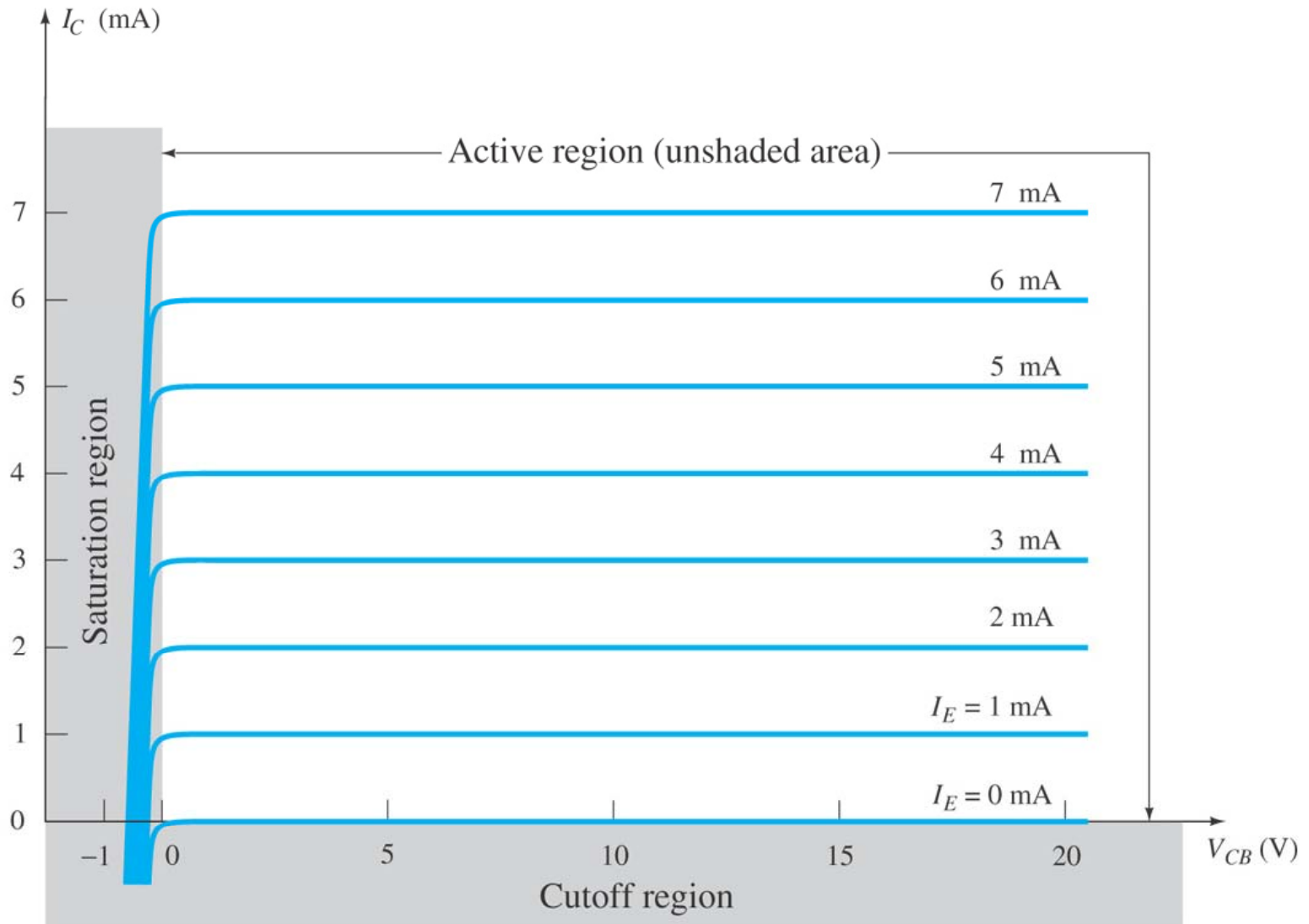

Problem 3.13

- Solution:
 - a) For $I_E = 4.5 \text{ mA}$ and $V_{CB} = 4 \text{ V}$, $I_C = 4.5 \text{ mA}$
 - b) For $I_E = 4.5 \text{ mA}$ and $V_{CB} = 16 \text{ V}$, $I_C = 4.5 \text{ mA}$
 - c) Negligible (not change – not depend on voltage)
 - d) $I_E = I_C$

Problem 3.15

- Question:
 - a) Given $\alpha = 0.998$, determine I_C if $I_E = 4 \text{ mA}$
 - b) Determine α if $I_E = 2.8 \text{ mA}$ and $I_B = 20 \text{ }\mu\text{A}$

Problem 3.15

- Solution:

a) $I_C = \alpha I_E = (0.998)(4m) = 3.993 \text{ mA}$





b) $I_E = I_C + I_B$
 $\therefore I_C = I_E - I_B = 2.8m - 20\mu = 2.78 \text{ mA}$

$$I_C = \alpha I_E$$

$$\therefore \alpha = \frac{I_C}{I_E} = \frac{2.78m}{2.8m} = 0.9929$$


CE Configuration

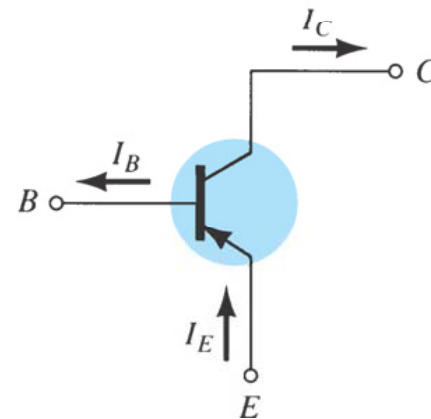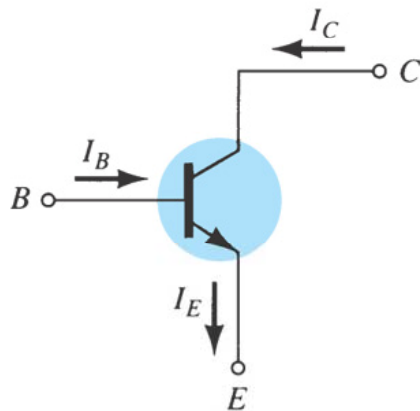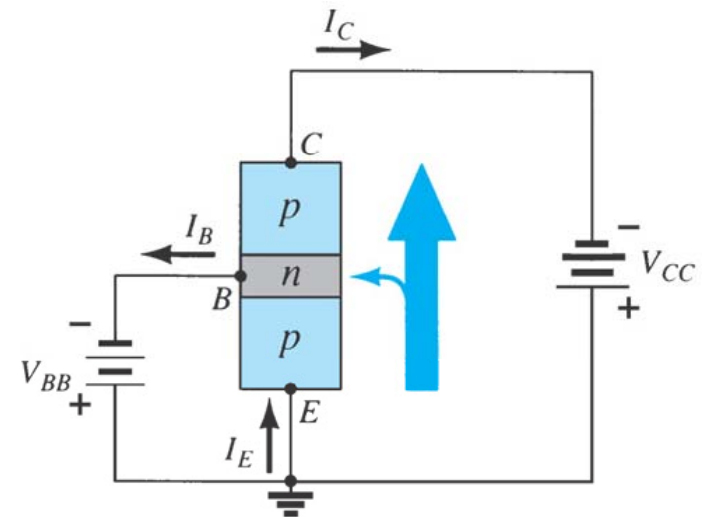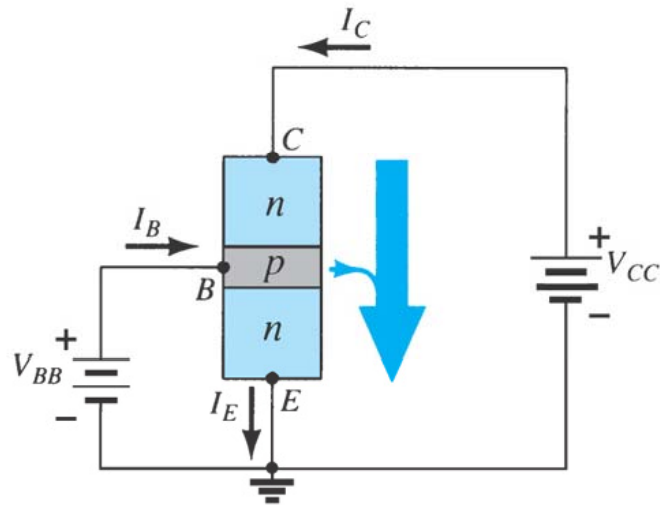- By applying the proper biasing and grounding the emitter terminal:




CE Configuration

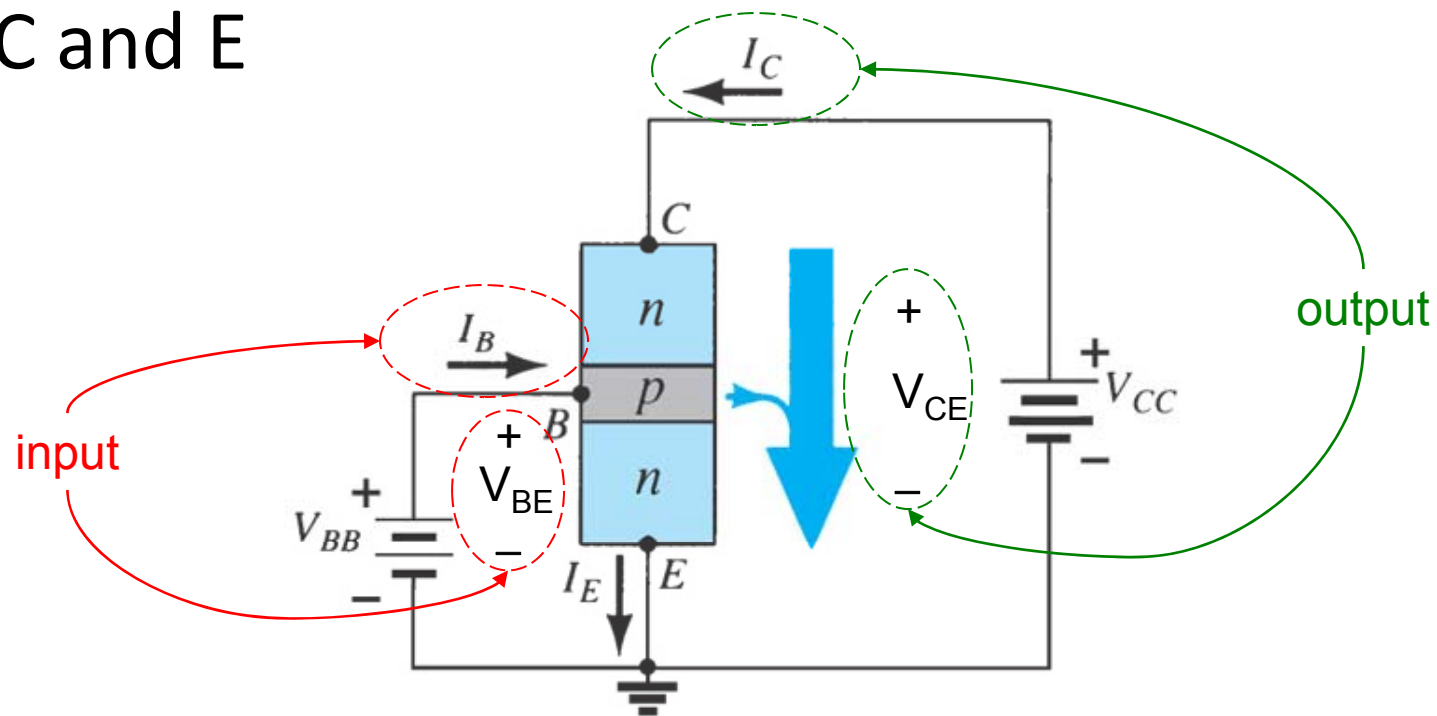- In CE configuration, the input terminal is between terminal B and E (due to ground at E)
- The output terminal is fixed between terminal C and E




CE Configuration

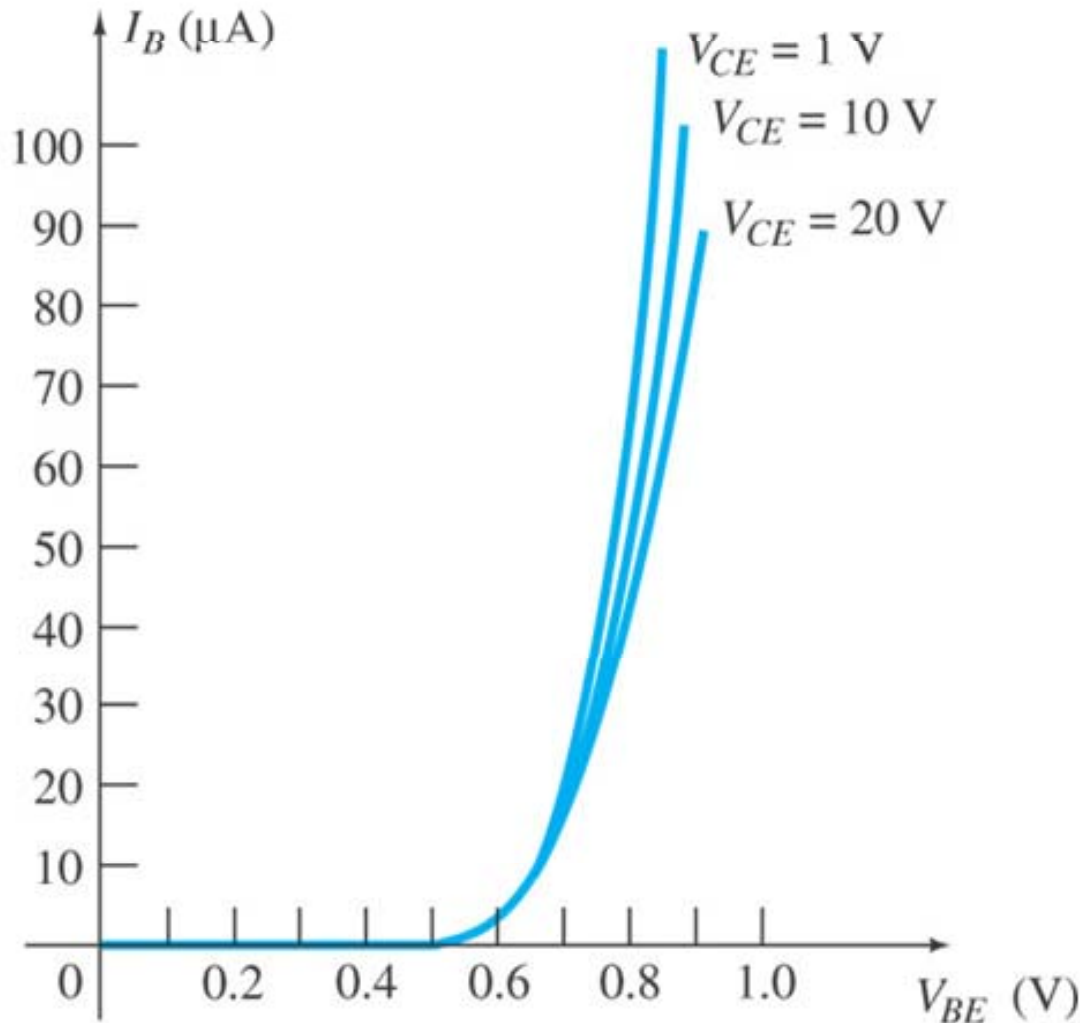

- By examining the input, plotting the V_{BE} and I_B , the output V_{CE} is fixed at $V_{BE} \approx 0.7 \text{ V}$ remains the same
- $V_{BE} = 0.7 \text{ V}$ is applied to all transistor configuration including this CE configuration
- $V_{EB} = 0.7 \text{ V}$ for pnp transistor

CE Configuration

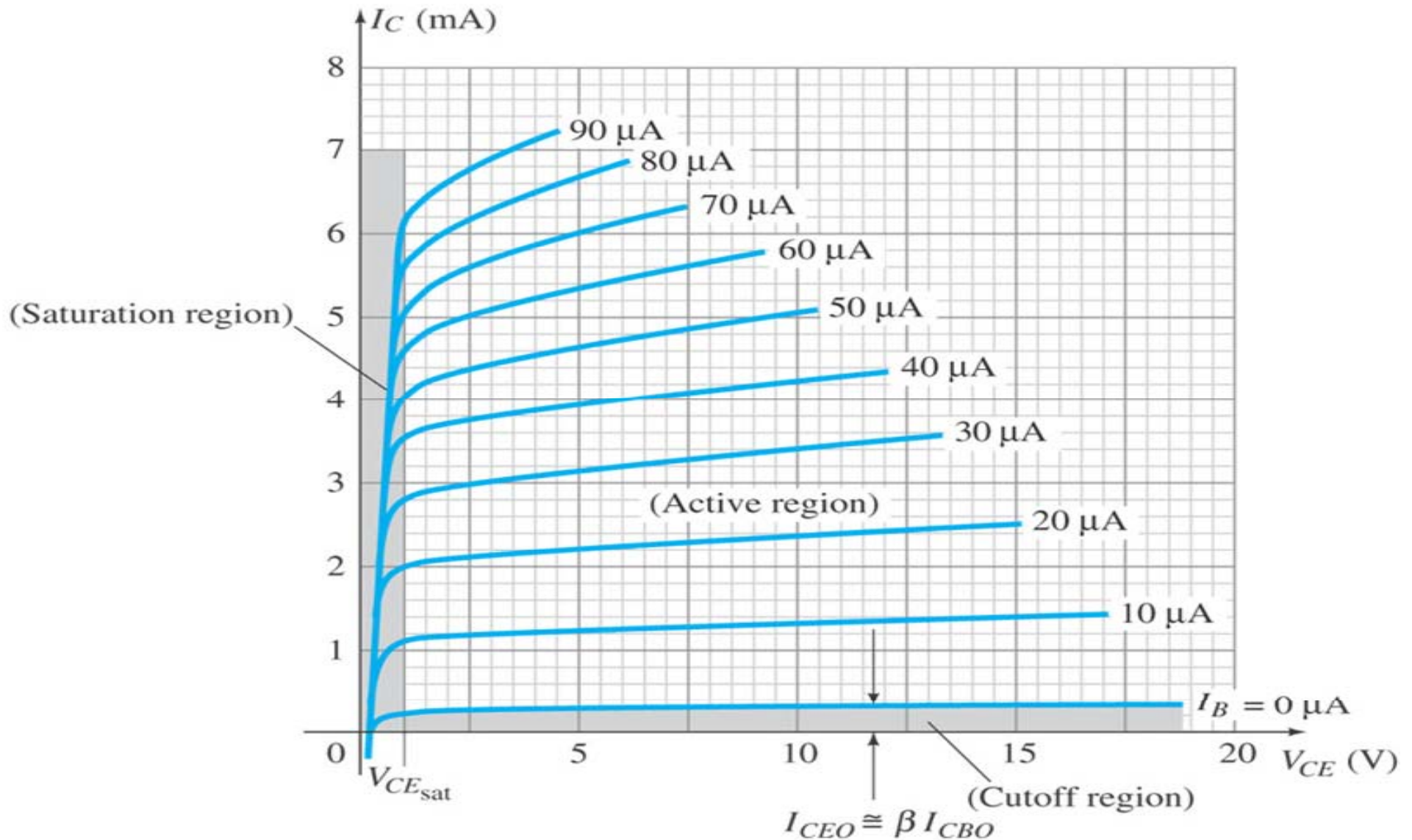- Examine the output at terminal C and E:



CE Configuration

- There are still 3 region of operation:
 - Active region
 - Cutoff region
 - Saturation region
- In active region, the relation between I_E and I_C is very different from the CB configuration
- This relation can be defined as:
$$I_C = \beta I_B$$
- where β is the ratio of I_C over I_B

CE Configuration

- The cutoff region remains the same with CB configuration, output (collector) current is zero (open-circuit equivalent):

$$I_C = 0 \text{ A}$$

- The saturation region also remains the same with CB configuration, output (collector-emitter) voltage is zero (short-circuit equivalent):

$$V_{CE} = 0 \text{ V}$$

Beta (β)

- From the equation $I_C = \beta I_B$, ratio of I_C over I_B is:

$$\beta = \frac{I_C}{I_B}$$

- β range from 50 to over 400
- For I_E , substitute the equation $I_E = I_C + I_B$ into the β equation:

$$I_E = \beta I_B + I_B = (\beta + 1)I_B$$

Beta (β) & Alpha (α)

- Substitute all of the equation in terms of β into the α equation:

$$\alpha = \frac{I_C}{I_E} = \frac{\beta I_B}{(\beta + 1)I_B} = \frac{\beta}{\beta + 1}$$


- For β in the terms of α :

$$\beta = \frac{\alpha}{1 - \alpha}$$

Problem 3.21

- Question:
 - a) For the CE characteristics in the figure given, find β at the operating point of $V_{CE} = +8\text{ V}$ and $I_C = 2\text{ mA}$
 - b) Find the value of α corresponding to this operating point


Problem 3.21

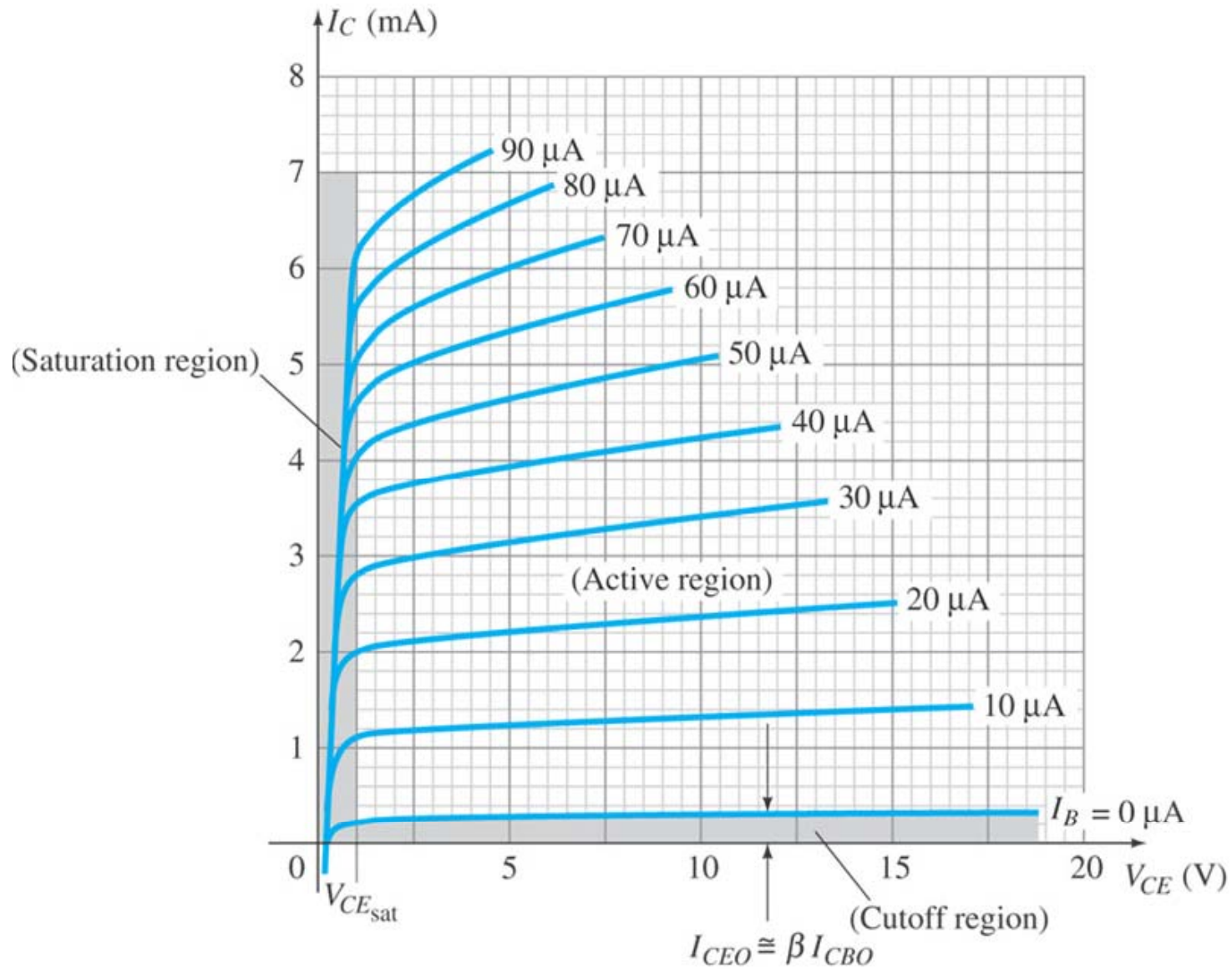

Problem 3.21

- Solution:
 - a) Plotting at the characteristic graph given the point $V_{CE} = +8 \text{ V}$ and $I_C = 2 \text{ mA}$:

$$\beta = \frac{I_C}{I_B} = \frac{2 \text{ mA}}{17 \mu\text{A}} = 117.65$$

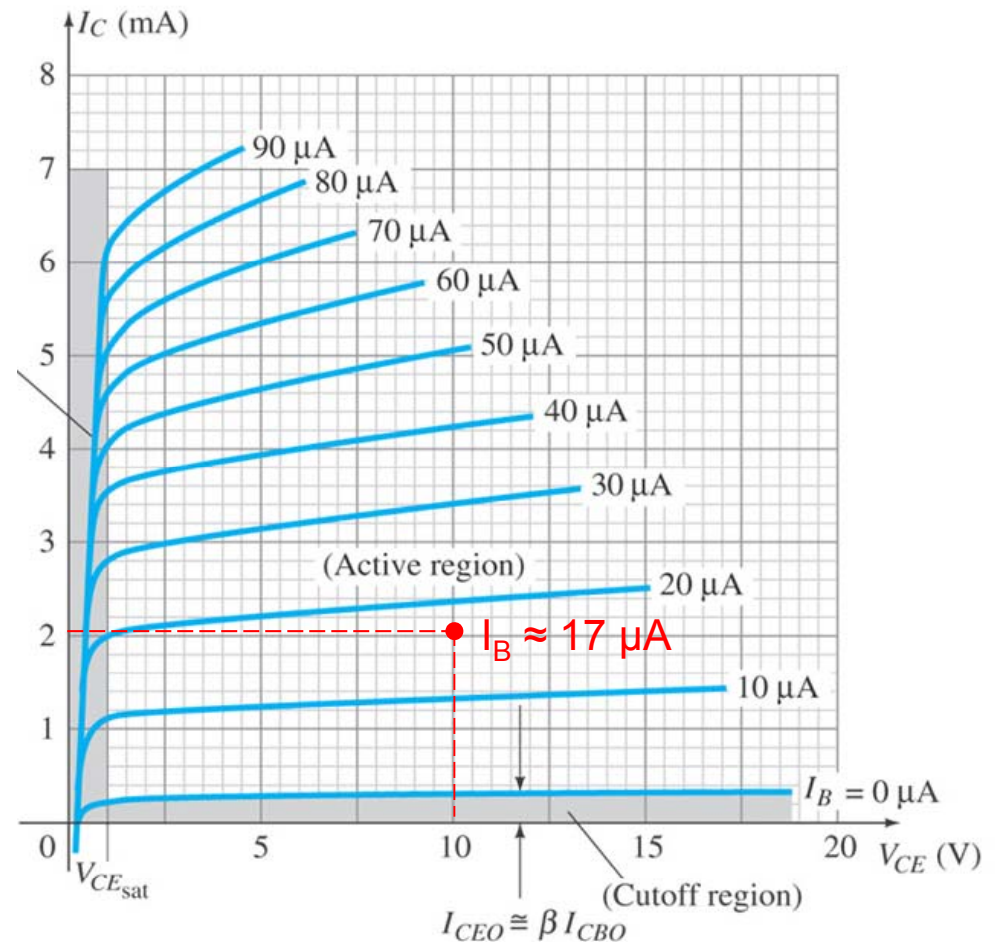

Problem 3.21

- Solution:


b) α can be obtained from β value:

$$\alpha = \frac{\beta}{\beta + 1} = \frac{117.65}{117.65 + 1} = 0.9916$$

Problem 3.25

- Question:
 - Using the characteristic given, determine β at $I_B = 25 \mu\text{A}$ and $V_{CE} = 10 \text{ V}$. Then calculate α and the resulting level of I_E
- Solution:
 - Find:
 - β
 - α
 - I_E


Problem 3.25

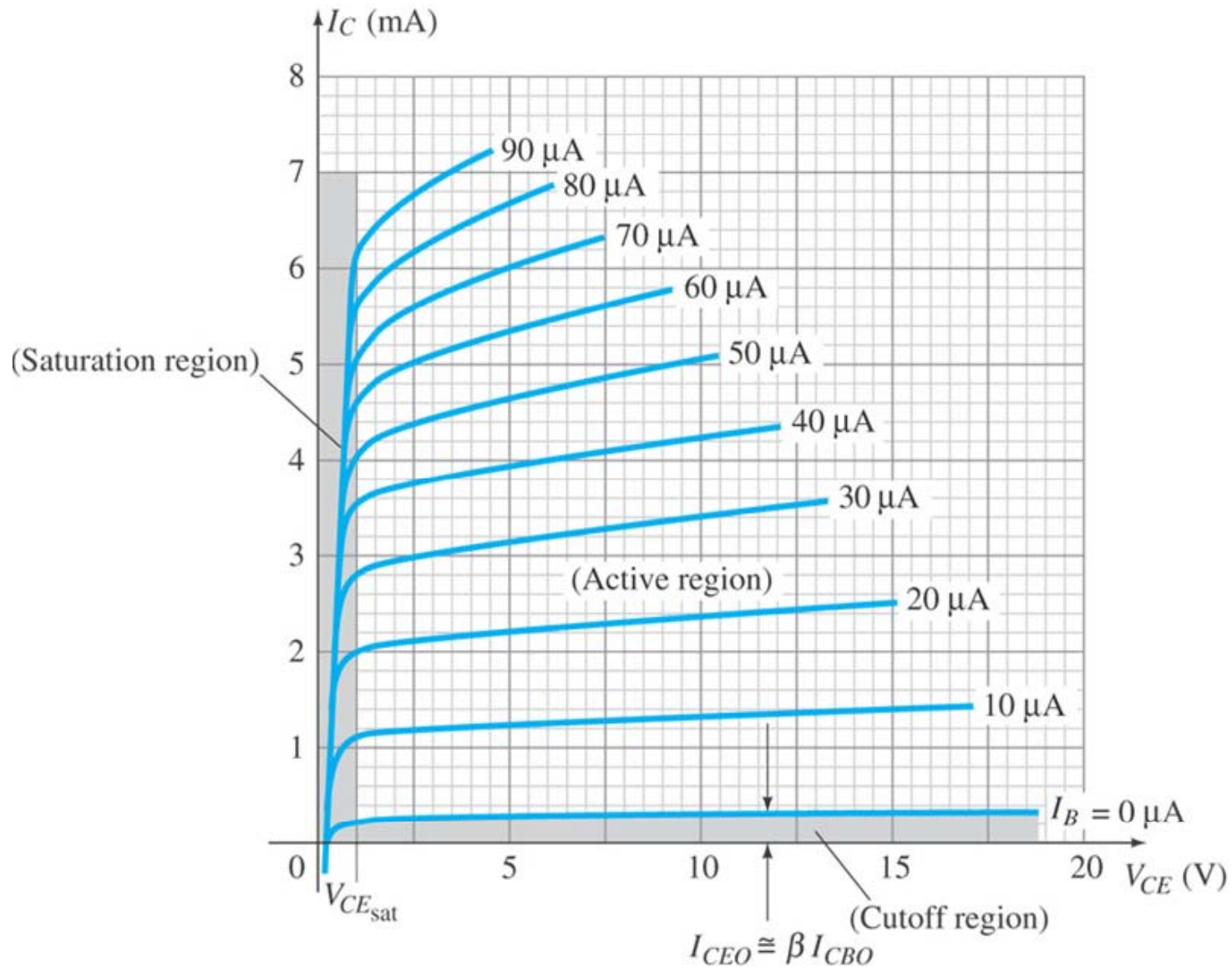

Problem 3.25

- Plotting at the characteristic graph given the point $V_{CE} = 10\text{ V}$ and $I_B = 25\ \mu\text{A}$:

$$\beta = \frac{I_C}{I_B} = \frac{2.9\text{ m}}{25\ \mu} = 116$$

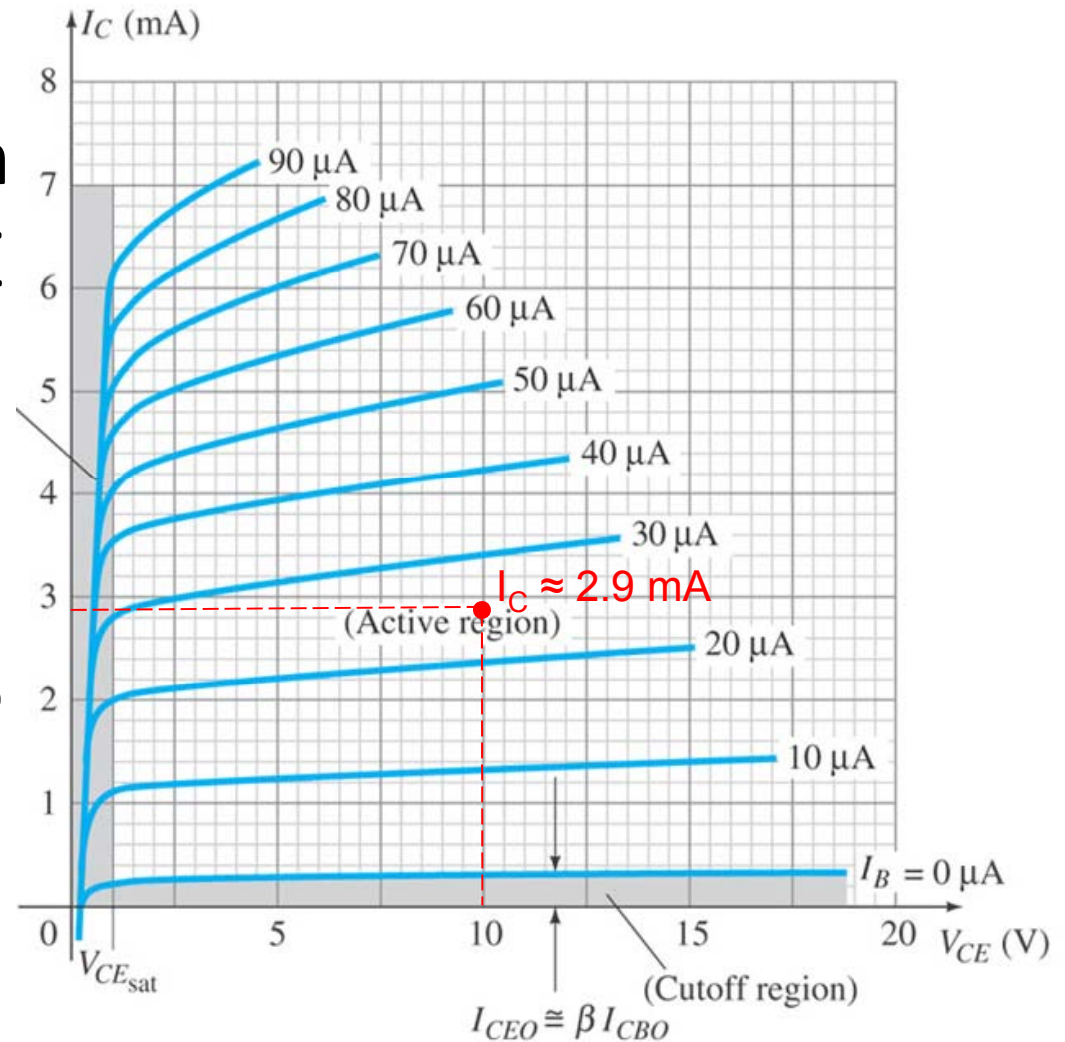

Problem 3.25

- α can be obtained from β value:


$$\alpha = \frac{\beta}{\beta + 1} = \frac{116}{116 + 1} = 0.9915$$

- I_E can be obtained from the α equation:

$$I_C = \alpha I_E$$
$$\therefore I_E = \frac{I_C}{\alpha} = \frac{2.9\text{m}}{0.9915} = 2.925 \text{ mA}$$


CC Configuration

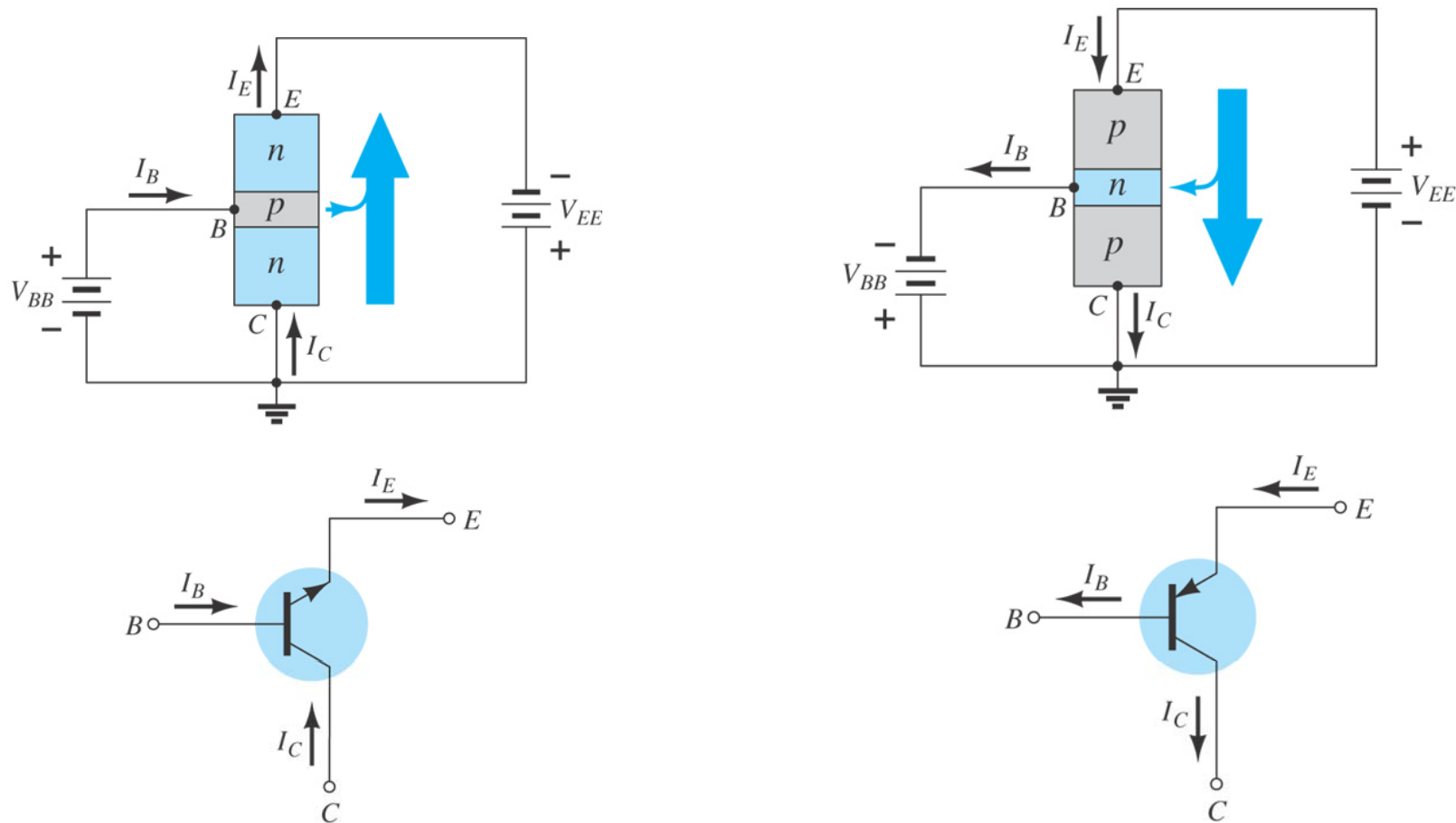- By applying the proper biasing and grounding the collector terminal:



CC Configuration

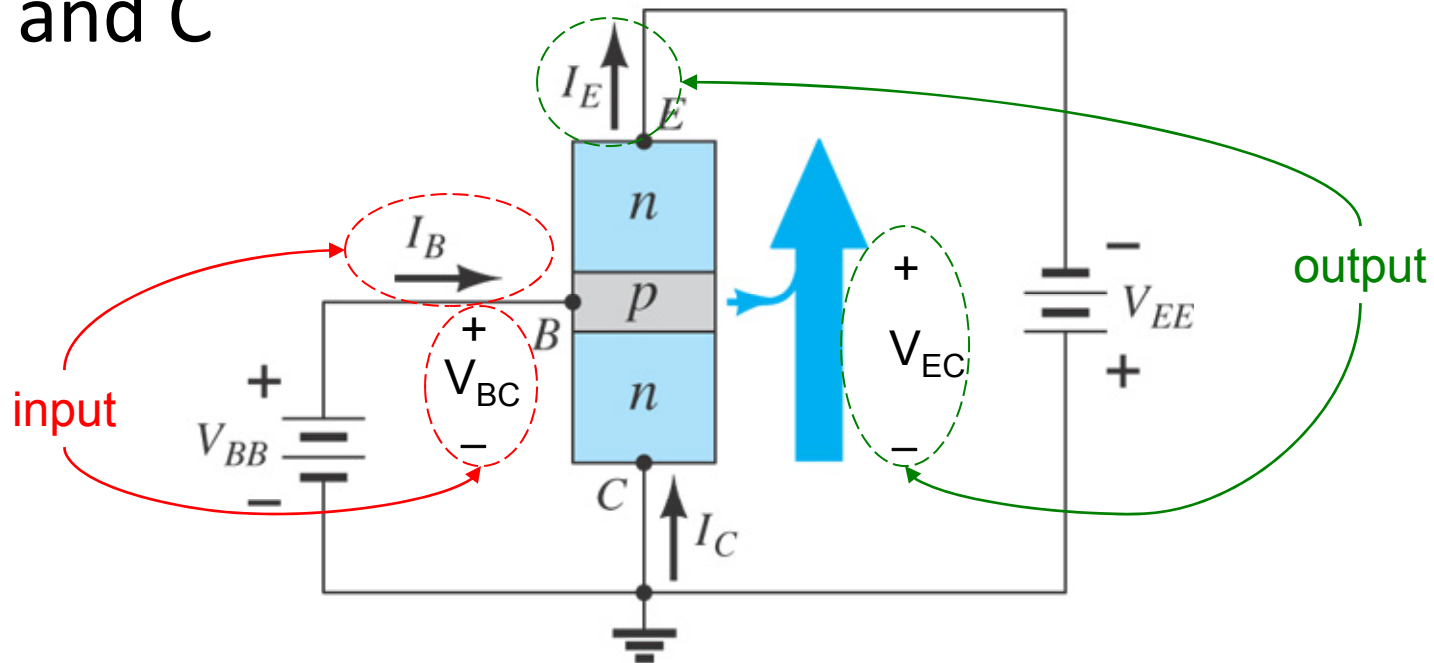- In CC configuration, the input terminal is between terminal B and C (due to ground at C)
- The output terminal is fixed between terminal E and C



CC Configuration

- By examining the input of CB and CE configuration, notice that they are the same ($V_{BE} = 0.7 \text{ V}$). As for that the input for CC configuration remains the same
- For CE the output voltage is V_{CE} while the output current is I_C . Meanwhile in CC, the output voltage is V_{EC} and the output current is I_E
- As for $I_C \approx I_E$ and $V_{CE} = V_{EC}$ (polarity change only), it is said that the characteristic of CE and CC configuration are the same

Limits Of Operation

- For the common-emitter characteristics, the maximum dissipation level is defined by:

$$P_{C_{\max}} = V_{CE} I_C$$

- As for that, I_C and V_{CE} must be in these range to make sure their product doesn't exceed the maximum power dissipation:

cutoff region $I_{CEO} \leq I_C \leq I_{C_{\max}}$

saturation region $V_{CE_{sat}} \leq V_{CE} \leq V_{CE_{\max}}$

$$V_{CE} I_C \leq P_{C_{\max}}$$

Limits Of Operation

- For example, if a transistor's collector power dissipation is specified to 300 mW with $I_{C_{max}} = 50$ mA and $V_{CE_{max}} = 20$ V
- For $I_{C_{max}}$ value, VCE would be: $I_C = \frac{P_C}{V_{CE_{max}}} = \frac{300m}{20} = 15$ mA
- For $V_{CE_{max}}$ value, I_C would be:

$$V_{CE} = \frac{P_C}{I_{C_{max}}} = \frac{300m}{50m} = 6 \text{ V}$$

- Adding two more points to complete the curve:

$$I_C = 30 \text{ mA}$$


$$\therefore V_{CE} = \frac{P_C}{I_C} = \frac{300m}{30m} = 10 \text{ V}$$

$$I_C = 25 \text{ mA}$$

$$\therefore V_{CE} = \frac{P_C}{I_C} = \frac{300m}{25m} = 12 \text{ V}$$

Limits Of Operation

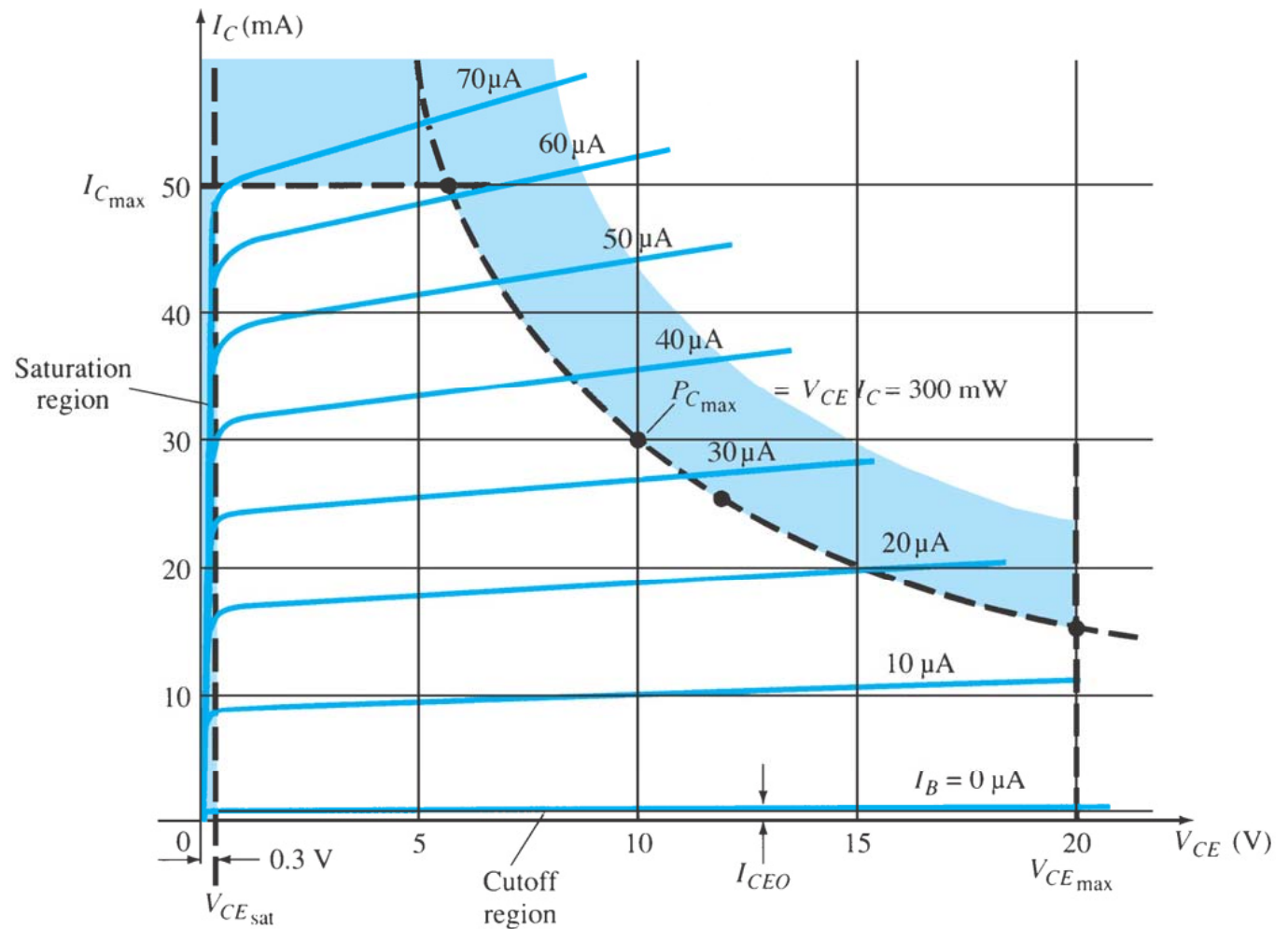- Connects all the points obtained, the curve becomes:



Limits Of Operation

- The same goes for a common-base configuration, its maximum power is defined as:

$$P_{C_{\max}} = V_{CB} I_C$$

- And the IC and VCE range is defined as:

$$I_{CEO} \leq I_C \leq I_{C_{\max}}$$

$$V_{CB_{sat}} \leq V_{CB} \leq V_{CB_{\max}}$$

$$V_{CB} I_C \leq P_{C_{\max}}$$

Transistor Datasheet

- Some of the important specification columns are bolded

V_{CEmax} I_{Cmax}

MAXIMUM RATINGS

Rating	Symbol	2N4123	Unit
Collector-Emitter Voltage	V_{CEO}	30	Vdc
Collector-Base Voltage	V_{CBO}	40	Vdc
Emitter-Base Voltage	V_{EB0}	5.0	Vdc
Collector Current – Continuous	I_C	200	mA dc
Total Device Dissipation @ $T_A = 25^\circ\text{C}$ Derate above 25°C	P_D	625 5.0	mW mW/°C
Operating and Storage Junction Temperature Range	T_J, T_{stg}	-55 to +150	°C

THERMAL CHARACTERISTICS

Characteristic	Symbol	Max	Unit
Thermal Resistance, Junction to Case	$R_{\theta JC}$	83.3	°C/W
Thermal Resistance, Junction to Ambient	$R_{\theta JA}$	200	°C/W

P_{Cmax}

2N4123
CASE 29-04, STYLE 1
TO-92 (TO-226AA)

3 Collector
2 Base
1 Emitter

**GENERAL PURPOSE
TRANSISTOR**
NPN SILICON

Transistor Datasheet

ELECTRICAL CHARACTERISTICS ($T_A = 25^\circ\text{C}$ unless otherwise noted)

Characteristic	Symbol	Min	Max	Unit
OFF CHARACTERISTICS				
Collector-Emitter Breakdown Voltage (1) ($I_C = 1.0\text{ mAdc}$, $I_E = 0$)	$V_{(BR)CEO}$	30		Vdc
Collector-Base Breakdown Voltage ($I_C = 10\text{ }\mu\text{Ade}$, $I_E = 0$)	$V_{(BR)CBO}$	40		Vdc
Emitter-Base Breakdown Voltage ($I_E = 10\text{ }\mu\text{Ade}$, $I_C = 0$)	$V_{(BR)EBO}$	5.0	–	Vdc
Collector Cutoff Current ($V_{CE} = 20\text{ Vdc}$, $I_E = 0$)	I_{CBO}	–	50	nAde
Emitter Cutoff Current ($V_{BE} = 3.0\text{ Vdc}$, $I_C = 0$)	I_{EBO}	–	50	nAde

I_{CBO} (cutoff) for common-base

I_{CEO} (cutoff) for common-emitter

Transistor Datasheet

ELECTRICAL CHARACTERISTICS ($T_A = 25^\circ\text{C}$ unless otherwise noted)

Characteristic	Symbol	Min	Max	Unit
ON CHARACTERISTICS				
DC Current Gain(1) ($I_C = 2.0 \text{ mAdc}$, $V_{CE} = 1.0 \text{ Vdc}$) ($I_C = 50 \text{ mAdc}$, $V_{CE} = 1.0 \text{ Vdc}$)	h_{FE}	50 25	150 -	-
Collector-Emitter Saturation Voltage(1) ($I_C = 50 \text{ mAdc}$, $I_B = 5.0 \text{ mAdc}$)	$V_{CE(sat)}$	-	0.3	Vdc
Base-Emitter Saturation Voltage(1) ($I_C = 50 \text{ mAdc}$, $I_B = 5.0 \text{ mAdc}$)	$V_{BE(sat)}$	-	0.95	Vdc
SMALL-SIGNAL CHARACTERISTICS				
Current-Gain – Bandwidth Product ($I_C = 10 \text{ mAdc}$, $V_{CE} = 20 \text{ Vdc}$, $f = 100 \text{ MHz}$)	f_T	250		MHz
Output Capacitance ($V_{CB} = 5.0 \text{ Vdc}$, $I_E = 0$, $f = 100 \text{ MHz}$)	C_{obo}	-	4.0	pF
Input Capacitance ($V_{BE} = 0.5 \text{ Vdc}$, $I_C = 0$, $f = 100 \text{ kHz}$)	C_{ibo}	-	8.0	pF
Collector-Base Capacitance ($I_E = 0$, $V_{CB} = 5.0 \text{ V}$, $f = 100 \text{ kHz}$)	C_{cb}	-	4.0	pF
Small-Signal Current Gain ($I_C = 2.0 \text{ mAdc}$, $V_{CE} = 10 \text{ Vdc}$, $f = 1.0 \text{ kHz}$)	h_{fe}	50	200	-
Current Gain – High Frequency ($I_C = 10 \text{ mAdc}$, $V_{CE} = 20 \text{ Vdc}$, $f = 100 \text{ MHz}$) ($I_C = 2.0 \text{ mAdc}$, $V_{CE} = 10 \text{ V}$, $f = 1.0 \text{ kHz}$)	h_{fe}	2.5 50	- 200	-
Noise Figure ($I_C = 100 \mu\text{A}$, $V_{CE} = 5.0 \text{ Vdc}$, $R_S = 1.0 \text{ k ohm}$, $f = 1.0 \text{ kHz}$)	NF	-	6.0	dB

β for DC

V_{CE} (saturation)

β for AC